

Hardware Modeling [VU] (191.011)

– WS25 –

From Circuits to Code and Back

Florian Huemer & Sebastian Wiedemann & Dylan Baumann



WS 2025/26

Lecture Goal

Develop an intuition for how VHDL code maps to hardware and the associated circuit complexity.

- Two examples
 - Circuit diagram $\rightarrow$ Derive VHDL code
 - VHDL code $\rightarrow$ Derive circuit diagram
- Important VHDL concepts used in the lecture
 - Sequential circuit elements
 - Behavioral modeling
 - Array-types and arithmetic functions

Example 1: Circuit $\rightarrow$ VHDL Code

  HWMMod
WS25

```
entity e is
  port (
    clk : in std_ulogic;
    res_n : in std_ulogic;
    ...
  );
end entity;

architecture a of e is
begin
  ...
end
```

Example 1: Circuit Diagram

HWMod
WS25

C2C

Introduction

Circuit → VHDL

Circuit


Entity

Architecture

Restructured

Architecture

VHDL → Circuit


 


Example 1 - Entity

HWMMod
WS25

C2C

Entity

  

```
1 entity circuit2code is
2   port (
3     clk : in std_ulogic;
4     res_n : in std_ulogic;
5     a : in std_ulogic;
6     b : in std_ulogic_vector(3 downto 0);
7     c : in std_ulogic_vector(3 downto 0);
8     d : in std_ulogic;
9     z : out std_ulogic_vector(3 downto 0)
10  );
```

Example 1 - Architecture

HWMod
WS25

C2C

Introduction

Circuit → VHDL

Circuit



Entity

Architecture

Restructured

Architecture

VHDL → Circuit

 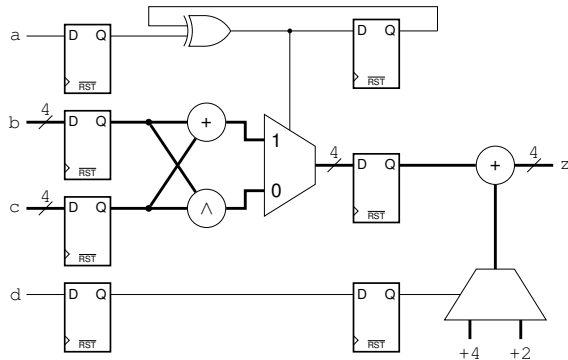

Architecture - Signal Declarations

HWMod
WS25

C2C

Introduction

Circuit → VHDL

Circuit


Entity

Architecture

Restructured

Architecture

VHDL → Circuit

 


```
1 architecture arch of circuit2code is
2   signal br, cr, y, yr :
3     std_ulogic_vector(3 downto 0);
4   signal ar, x, xr, dr, drr : std_ulogic;
5 begin
```

Architecture - Registers

HWMod
WS25

C2C

 Introduction
Circuit → VHDL
Circuit
Entity
Architecture
Restructured
Architecture
VHDL → Circuit



```
6  process (clk, res_n)
7  begin
8      if res_n = '0' then
9          ar <= '0'; dr <= '0';
10         xr <= '0'; drr <= '0';
11         br <= (others => '0');
12         cr <= (others => '0');
13         yr <= (others => '0');
14     elsif rising_edge(clk) then
15         ar <= a;
16         br <= b;
17         cr <= c;
18         dr <= d;
19         xr <= x;
20         yr <= y;
21         drr <= dr;
22     end if;
23 end process;
```

Architecture - Combinational Logic I

HWMod
WS25

C2C

Introduction

Circuit → VHDL

Circuit


Entity

Architecture

Restructured

Architecture

VHDL → Circuit

 


```
24  x <= ar xor xr;
25
26  process (all)
27  begin
28      if x = '1' then
29          y <= std_ulogic_vector(
30              unsigned(br) +
31              unsigned(cr)
32          );
33      else
34          y <= br and cr;
35      end if;
36  end process;
```

Architecture - Combinational Logic II

HWMod
WS25

C2C

 Introduction
Circuit → VHDL
Circuit
Entity
Architecture
Restructured
Architecture
VHDL → Circuit



```
37 process (all)
38     variable m : integer;
39 begin
40     if drr = '1' then
41         m := 2;
42     else
43         m := 4;
44     end if;
45
46     z <= std_ulogic_vector(
47         unsigned(yr) + m
48     );
49 end process;
50 end architecture;
```

Restructured Architecture

HWMod
WS25

C2C

Introduction

Circuit → VHDL

Circuit

Entity

Architecture

Restructured

Architecture

VHDL → Circuit

```
1  process (clk, res_n)
2  begin
3      if res_n = '0' then
4          ar <= '0'; dr <= '0';
5          xr <= '0'; drr <= '0';
6          br <= (others => '0');
7          cr <= (others => '0');
8          yr <= (others => '0');
9      elsif rising_edge(clk) then
10         ar <= a;
11         br <= b;
12         cr <= c;
13         dr <= d;
14         xr <= x;
15         yr <= y;
16         drr <= dr;
17     end if;
18 end process;

19 x <= ar xor xr;
20
21 process (all)
22 begin
23     if x = '1' then
24         y <= std_ulogic_vector(
25             unsigned(br) +
26             unsigned(cr)
27         );
28     else
29         y <= br and cr;
30     end if;
31 end process;
```

Restructured Architecture

HWMod
WS25

C2C

Introduction

Circuit → VHDL

Circuit

Entity

Architecture

Restructured
Architecture

VHDL → Circuit

```
1  process (clk, res_n)
2  begin
3      if res_n = '1' then
4          ar <= '0'; xr <= '0';
5          dr <= '0'; drr <= '0';
6          br <= (others => '0');
7          cr <= (others => '0');
8          yr <= (others => '0');
9      elsif rising_edge(clk) then
10         ar <= a;
11         br <= b;
12         cr <= c;
13         dr <= d;
14         xr <= x;
15         if x = '1' then
16             yr <= std_ulogic_vector(
17                 unsigned(br) +
18                 unsigned(cr)
19             );
20         else
21             yr <= br and cr;
22         end if;
23         drr <= dr;
24         end if;
25     end process;
26
27
28     x <= ar xor xr;
```

Restructured Architecture

HWMod
WS25

C2C

Introduction

Circuit → VHDL

Circuit

Entity

Architecture

Restructured
Architecture

VHDL → Circuit

```
1  process (clk, res_n)
2  begin
3      if res_n = '1' then
4          ar <= '0'; xr <= '0';
5          dr <= '0'; drr <= '0';
6          br <= (others => '0');
7          cr <= (others => '0');
8          yr <= (others => '0');
9      elsif rising_edge(clk) then
10         ar <= a;
11         br <= b;
12         cr <= c;
13         dr <= d;
14         xr <= ar xor xr;
15         if (ar xor xr) = '1' then
16             yr <= std_ulogic_vector(
17                 unsigned(br) +
18                 unsigned(cr)
19             );
```

```
20         else
21             yr <= br and cr;
22         end if;
23
24         drr <= dr;
25     end if;
26 end process;
27
28 process (all)
29     variable m : integer;
30 begin
31     if drr = '1' then
32         m := 2;
33     else
34         m := 4;
35     end if;
36     z <= std_ulogic_vector(
37         unsigned(yr) + m);
38 end process;
```

Example 2: VHDL Code → Circuit

HWMod
WS25

C2C

Introduction

Circuit → VHDL



VHDL → Circuit

Entity

Architecture

Circuit

```
entity e is  
  port (  
    clk : in std_ulogic;  
    res_n : in std_ulogic;  
    ...  
  );  
end entity;  
  
architecture a of e is  
  begin  
    ...  
  end  
end architecture;
```

  

Example 2: Entity

HWMod
WS25

C2C

Introduction

Circuit → VHDL

VHDL → Circuit

Entity

Architecture

Circuit

```
1 entity code2circuit is
2     generic (
3           : positive
4     );
5     port (
6         clk : in std_ulogic;
7         res_n : in std_ulogic;
8         a : in std_ulogic;
9         
10        
11        
12        x : out std_ulogic;
13        
14    );
15 end entity;
```

Example 2: Architecture

HWMod
WS25

C2C

Introduction

Circuit → VHDL

VHDL → Circuit

Entity

Architecture

Circuit

```
1 architecture arch of code2circuit is
2     signal r0, r1 : std_ulogic;
3     signal r2 : c'subtype;
4 begin
5     process (clk, res_n)
6     begin
7         if res_n = '0' then
8             r0 <= '0'; r1 <= '0'; x <= '0';
9             r2 <= (others => '0');
10        elsif rising_edge(clk) then
11            r0 <= a xor r1;
12            r1 <= r0;
13            x <= r1;
14            r2 <= std_ulogic_vector(
15                signed(c) + signed(d)
16            );
17        end if;
18    end process;
19    process(all)
20        variable temp : std_ulogic;
21    begin
22        temp := '0';
23        for i in b'range loop
24            temp := temp or b(i);
25        end loop;
26
27        y <= r2;
28
29        if temp and r0 then
30            y <= std_ulogic_vector(
31                to_unsigned(3, y'length)
32            );
33        end if;
34    end process;
35
36 end architecture;
```

Example 2: Circuit - Registers

HWMod
WS25

C2C

Introduction

Circuit → VHDL


VHDL → Circuit

Entity

Architecture

Circuit

```
1 architecture arch of code2circuit is
2   signal r0, r1 : std_ulogic;
3   signal r2 : c'subtype;
4 begin
5   process (clk, res_n)
6   begin
7     if res_n = '0' then
8       r0 <= '0'; r1 <= '0'; x <= '0';
9       r2 <= (others => '0');
10    elsif rising_edge(clk) then
11      r0 <= a xor r1;
12      r1 <= r0;
13      x <= r1;
14      r2 <= std_ulogic_vector(
15        signed(c) + signed(d)
16      );
17    end if;
18  end process;
```

 

Example 2: Circuit - Combinational Process

HWMod
WS25

C2C

Introduction

Circuit → VHDL


VHDL → Circuit

Entity

Architecture

Circuit
 
```
19  process(all)
20      variable temp : std_ulogic;
21  begin
22      temp := '0';
23      for i in b'range loop
24          temp := temp or b(i);
25      end loop;
26
27      y <= r2;
28
29      if temp and r0 then
30          y <= std_ulogic_vector(
31              to_unsigned(3, y'length)
32          );
33      end if;
34  end process;
35
36  end architecture;
```



Lecture Complete!