

Hardware Modeling [VU] (191.011)

– WS25 –

Circuit Description with Entities and Architectures


Florian Huemer & Sebastian Wiedemann & Dylan Baumann

WS 2025/26

Introduction

HWMod
WS25

 Ent. & Arch.
Introduction
Entities
Architectures



Recall



Not everything in VHDL is synthesizable.

Entities

HWMod
WS25

Ent. & Arch.
Introduction
Entities
Ports
Generics
Unconstrained
Types
Architectures

  - Interface specification of a module
 - Interface signals
 - Parameters
- No internal behavior specified
- Multiple different architectures possible
- Analogies



Entities (cont'd)

■ Entity declaration syntax

```
entity NAME is
  [ generic ( {generic_element;} generic_element ); ]
  [ port ( {port_element;} port_element ); ]
  [ entity_declarative_part ]
  [ begin entity_statement_part ]
end entity;
```

- Generic clause: configuration/parameters
- Port clause: physical I/O signals
- Declarations: constants, types, subprograms, etc.
- Statements: parameter checks

Ports

HWMod
WS25

Ent. & Arch.
Introduction
Entities
Ports
Generics
Unconstrained
Types
Architectures

■ Port element declaration syntax


```
port_element ::=  
    PORT_NAME : [mode] DATA_TYPE [:= default_value]
```

■ Mode

- Possible Values: `in`, `out`, `inout`, `buffer`, `linkage`
- Default (if mode is omitted): `in`
- Defines the direction of a signal (can it be read, written or both)

■ Example entity
 
```
1 entity and_gate is  
2 port (  
3     a : in boolean;  
4     b : in boolean;  
5     x : out boolean -- no semicolon here!  
6 );  
7 end entity;
```




- Generic element declaration syntax

```
generic_element ::=  
    GENERIC_NAME : DATA_TYPE [:= default_value]
```

- No mode required (all generics are “constant inputs”)
- Basically constants in the architecture
- Example entity
 
```
1 entity and_gate is  
2   generic (  
3     N : integer := 2  
4   );  
5   port (  
6     i : in boolean_vector(N-1 downto 0);  
7     x : out boolean  
8   );  
9 end entity;
```



Unconstrained Types

HWMod
WS25

Ent. & Arch.
Introduction
Entities
Ports
Generics
Unconstrained
Types
Architectures

■ Unconstrained generic example

```
1 entity cpu is
2   generic (
3     ENABLE_BRANCH_PREDICTION : string := "YES"; -- "NO"
4     [...]
5   );
6   [...]
7 end entity;
```

■ Unconstrained port example

```
1 entity and_gate is
2   port (
3     i : in boolean_vector;
4     x : out boolean
5   );
6 end entity;
```

Architectures

- VHDL standard  :

“An architecture body defines the body of a design entity.”

- Contains the actual circuit description

- Architecture declaration syntax

```
architecture NAME of ENTITY_NAME is
    architecture_declarative_part
begin
    architecture_statement_part
end architecture;
```

- Declarative/statement part

```
architecture_declarative_part ::= 
    { block_declarative_item }
architecture_statement_part ::= 
    { concurrent_statement }
```

Architecture (cont'd)

HWMOD
WS25

Ent. & Arch.
Introduction
Entities
Architectures
Concurrent
Assignments
Signal Declarations


- Declarative part (block declarative items) 
 - Signals
 - Constants
 - Types
 - Sub-programs
 - etc.
- Statement part (concurrent statements) 
 - **Concurrent signal assignments**
 - Processes
 - Instantiation statements
 - Blocks statements
 - Generate statements
 - etc.

Concurrent Signal Assignments – Example: AND gate

HWMod
WS25

Ent. & Arch.
Introduction
Entities
Architectures
Concurrent
Assignments
Signal Declarations
 
```
1 entity and_gate is
2   port (
3     a : in boolean;
4     b : in boolean;
5     x : out boolean
6   );
7 end entity;
8
9 architecture arch of and_gate is
10 begin
11   x <= a and b;
12 end architecture;
```




Concurrent Signal Assignments – Example: Multiplexer

HWMod
WS25

Ent. & Arch.
Introduction
Entities
Architectures
Concurrent
Assignments
Signal Declarations

```
1 entity mux41 is
2   port (
3     c : in boolean_vector(1 downto 0);
4     i : in boolean_vector(3 downto 0);
5     o : out boolean
6   );
7 end entity;
8
9 architecture arch of mux41 is
10 begin
11   o <= i(0) when not c(1) and not c(0) else
12     i(1) when not c(1) and      c(0) else
13     i(2) when      c(1) and not c(0) else
14     i(3) when      c(1) and      c(0);
15 end architecture;
```

 

Signal Declarations

- Signal declaration syntax

```
signal NAME : DATA_TYPE [ := default_value ] ;
```

- Signals vs. variables

Signals

- Declaration: (as) ports, entities, architectures, packages
- Assignment: deferred (event queue)
- Assignment operator: <=


Variables

- Declaration: subprograms, processes
- Assignment: immediate
- Assignment operator: :=

 Example - Full Adder

HWMod
WS25

Ent. & Arch.
Introduction
Entities
Architectures
Concurrent
Assignments
Signal Declarations



Important

The order of statements in an architecture carries **no** semantic significance!

```
1 entity fa is
2 port (
3   a, b, cin : in boolean;
4   sum, cout : out boolean
5 );
6 end entity;
7
8 architecture arch of fa is
9 signal x, y, z : boolean;
10 begin
11   x <= a xor b;
12   y <= a and b;
13   sum <= cin xor x;
14   z <= cin and x;
15   cout <= y or z;
16 end architecture;
```

Lecture Complete!