Circuit Description with Entities and Architectures

Hardware Modeling [VU] (191.011)
—WS25—
Grout Decorption with Entitles and Architectures
Florian Humer & Schastlan Wedemann & Dylan Baumann

Now that we have some basic knowledge about the programming language VHDL, we will take a look at how it is actually used to describe hardware.





Hardware Modeling [VU] (191.011) - WS25 -

Circuit Description with Entities and Architectures

Florian Huemer & Sebastian Wiedemann & Dylan Baumann

WS 2025/26

Circuit Description with Entities and Architectures
Introduction
Introduction




Recall that, only a subset of the language features in VHDL is synthesizable. This means that only this subset can be used to actually describe hardware. Nevertheless, the non-synthesizable parts of the language are vitally important to, for example, verify the behavior of a design in a testbench. So far we have treated VHDL as just another, maybe a little exotic, programming language. Now, we want to focus on the circuit-level semantics of its language constructs. At the end of the lecture, we will have implemented our first combinational digital circuit.

Introduction

HWMod WS25

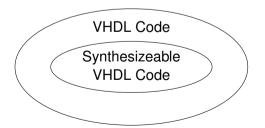Ent. & Arch.
Introduction
Entities
Architectures



Recall

Not everything in VHDL is synthesizable.

Circuit Description with Entities and Architectures
Entities
Entities

Interface specification of a module
Interface signals
Parameters

When designing a circuit, one of the key tasks is to define its interface to the outside world. As already introduced in a previous lecture, in VHDL this is done using the entity-construct. It defines the inputs, outputs, and configuration parameters of a module.

Entities

HWMod WS25

- Ent. & Arch.
 Introduction
 Entities
 Ports
 Generics
 Unconstrained
 Types
- Interface specification of a module
 - Interface signals
 - Parameters

Interface specification of a module
Interface signals
Parameters
No internal behavior specified

However, it does not specify how the module behaves internally – that is handled by its architectures.

Entities



- Ent. & Arch.
 Introduction
 Entities
 Ports
 Generics
 Unconstrained
 Types
- Interface specification of a module
 - Interface signals
 - Parameters
- No internal behavior specified

└─Circuit Description with Entities and Architectures
└─Entities
└─Entities

Interface specification of a module
Interface signals
Interface s

Note that a single entity can have multiple different architectures.

Entities

- HWMod WS25
- Ent. & Arch.
 Introduction
 Entitles
 Ports
 Generics
 Unconstrained
 Types
- Interface specification of a module
 - Interface signals
 - Parameters
- No internal behavior specified
- Multiple different architectures possible

-Circuit Description with Entities and Architectures **Entities Entities**




To draw a comparison to other programming languages, the entity-architecture concept can be compared to abstract classes or interfaces and their implementations. However, unlike interfaces in for example Java or C# an architecture can only have a single entity.

Entities

- **HWMod** WS25
- Entities
- Interface signals Parameters
- No internal behavior specified

■ Interface specification of a module

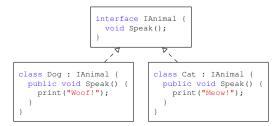- Multiple different architectures possible
- Analogies



☐ Circuit Description with Entities and Architectures ☐ Entities ☐ Entities




Another analogy closer to hardware – that fits slightly better – is the picture of a microchip and its socket. The socket represents the interface, while the actual microchip can be changed – for example to different compatible processors with varying performance levels.


Entities

HWMod WS25

Ent. & Arch.
Introduction
Entities
Ports
Generics
Unconstrained
Types

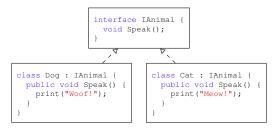- Interface specification of a module
 - Interface signals
 - Parameters
- No internal behavior specified
- Multiple different architectures possible
- Analogies



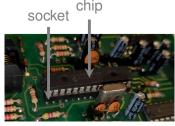

```
Brity decimation system

sensity MAME is

{ peneral ( (speneric_wlement) peneric_wlement ); }

{ pent ( print ( print_wlement) pent_wlement ); }

{ buyle sensity_statement_part }

send sensity_
```

Entities are declared using the entity keyword, followed by an identifier representing its name and the keyword is. Then four blocks referred to as the generics and ports clause and the entity declarative and statement parts are listed. Note that, as explicitly marked in the syntax specification, each of these blocks is optional. We have already seen this in previous code examples, where only completely empty entities have been used so far.

Entities (cont'd)



HWMod WS25

Ent. & Arch.
Introduction
Entities
Ports
Generics
Unconstrained
Types

```
entity NAME is
  [ generic ( {generic_element; } generic_element ); ]
  [ port ( {port_element; } port_element ); ]
  [ entity_declarative_part ]
  [ begin entity_statement_part ]
end entity;
```

```
☐ Circuit Description with Entities and Architectures ☐ Entities (cont'd)
```

The generic clause is introduced with the generic keyword, which is followed by a semicolon-separated list of generic elements wrapped in parentheses. Note that in VHDL-2008 and earlier revisions the last element in the list is not terminated with a semicolon. Having an additional semicolon at this position is only allowed since VHDL-2019 – in all older versions this syntax leads to a compilation error. Generics can be used to define parameters that customize the behavior or structure of a module, improving code reuse and flexibility. We will go into further depth on generics on a following slide.

Entities (cont'd)



HWMod WS25

Ent. & Arch.
Introduction
Entities
Ports
Generics
Unconstrained
Types

Entity declaration syntax

```
entity NAME is
  [ generic ( {generic_element;} generic_element ); ]
  [ port ( {port_element;} port_element ); ]
  [ entity_declarative_part ]
  [ begin entity_statement_part ]
end entity;
```

■ Generic clause: configuration/parameters

```
└─Circuit Description with Entities and Architectures └─Entities (cont'd)
```

The port clause is marked with the port keyword and is then followed by a list of port elements using the same syntax as the generic block. As for the generics, the last element of the list is "NOT" followed by a semicolon. The signals defined in and entity's port list define the actual physical interface of the module to the outside world. If you recall the Java and C# analogies from before, you can view the ports as the methods of an abstract class, and the generics as the parameters of the constructor.

Entities (cont'd)



HWMod WS25

Ent. & Arch.
Introduction
Entities
Ports
Generics
Unconstrained
Types

```
entity NAME is
  [ generic ( {generic_element;} generic_element ); ]
  [ port ( {port_element;} port_element ); ]
  [ entity_declarative_part ]
  [ begin entity_statement_part ]
end entity;
```

- Generic clause: configuration/parameters
- Port clause: physical I/O signals

```
└─Circuit Description with Entities and Architectures

└─Entities

└─Entities (cont'd)
```

```
# Enthy declaration system

in the production of the production of
```

As the name suggest the declarative parts simply contains a range of declarations for – among other things – constants, types, or subprograms. The objects declared here are visible only to the architectures implementing the respective entity.

Entities (cont'd)



HWMod WS25

Ent. & Arch.
Introduction
Entities
Ports
Generics
Unconstrained
Types

```
entity NAME is
  [ generic ( {generic_element;} generic_element ); ]
  [ port ( {port_element;} port_element ); ]
  [ entity_declarative_part ]
  [ begin entity_statement_part ]
end entity;
```

- Generic clause: configuration/parameters
- Port clause: physical I/O signals
- Declarations: constants, types, subprograms, etc.

```
└─Circuit Description with Entities and Architectures └─Entities (cont'd)
```

```
| Sirtly declaration syntax
| mainty MADE is
| Spenserie (!spenserie_alement) | generie_alement ); ]
| Sentity_declarative_part |
| Simple mainty_seriesment_part |
| Simple mainty_seriesment_part |
| Sentity_declarative_part |
| Sentity_declarative_part |
| Sentity_declarative_part |
| Sentity_declarative_part |
```

Finally, the begin keyword introduces the statement part, which can for instance be used to implement constraints or static sanity checks on the generic parameters.

Entities (cont'd)



HWMod WS25

Ent. & Arch.
Introduction
Entities
Ports
Generics
Unconstrained
Types

```
entity NAME is
  [ generic ( {generic_element; } generic_element ); ]
  [ port ( {port_element; } port_element ); ]
  [ entity_declarative_part ]
  [ begin entity_statement_part ]
end entity;
```

- Generic clause: configuration/parameters
- Port clause: physical I/O signals
- Declarations: constants, types, subprograms, etc.
- Statements: parameter checks



POrt element declaration syntax
 port_element ::=
 PORT_NAME : [mode] DATA_TYPE [:= default_value]

OK, let's start with taking a closer look at the ports section. The declaration of port elements looks very similar to the declaration of variables or constants we have already seen in previous lectures. Each port element starts with a name, followed by a colon and the optional mode specifier. Then the datatype of the port is specified. Finally, an optional default value can be added. The semantics of this will be explained in an upcoming lecture. Note that similar to variable or constant declarations the port name can also be a comma-separated list of identifiers. The semantics of this syntax should be obvious.

Ports

HWMod WS25

Ent. & Arch.
Introduction
Entities
Ports
Generics
Unconstrained
Types

■ Port element declaration syntax

```
port_element ::=
  PORT_NAME : [mode] DATA_TYPE [:= default_value]
```


Port element declaration syntax

PORT_MADME : [mode] DATA_TYPE [:= default_value]

POSSEN WARDS: in, out, innot, buffer, linkege

Detail (fimed) is omthod; in

The mode of a port basically specifies its direction. The VHDL standard defines five possible modes, with "in" being the default one. However, in this course we will only use the first three – that is in, out and inout. The other ones are rarely used and will therefore not be covered in this course. As you might be able to deduce from the mode names, "in" and "out" define circuit inputs and outputs, respectively. The mode inout is only used for interface signals that are actively driven by the design as well as read back. This is for example required to implement open-drain outputs or bus protocols where it is required to disconnect from a shared bus wire because other devices actively drive it. However, for now we will just use the modes "in" and "out". The inout mode will be covered in more detail in an upcoming lecture. In the context of synthesizable entities the port datatype must of course be a synthesizable datatype, such as boolean, bit or integer. Although it seems very natural to represent the logical binary state of a signal wire using a Boolean value, in practice these datatypes are rarely used for interface signals. As will be shown in an upcoming lecture, even in a digital system it is beneficial to model more signal states than just high and low. An example where the boolean values are insufficient is the shared bus wire we just mentioned. However, until we learn about more specialized datatypes, we will stick to Booleans.

Ports

HWMod WS25

■ Port element declaration syntax

```
port_element ::=
  PORT_NAME : [mode] DATA_TYPE [:= default_value]
```

- Mode
 - Possible Values: in, out, inout, buffer, linkage
 - Default (if mode is omitted): in
 - Defines the direction of a signal (can it be read, written or both)

☐ Circuit Description with Entities and Architectures ☐ Entities ☐ Ports



The example entity AND-gate on this slide, has two inputs – named a and b – and one output x. As its name suggests this entity models the interface of a 2-input "and" gate. We will add an appropriate architecture on an upcoming slide.

Ports

HWMod WS25

Ent. & Arch.
Introduction
Entities
Ports
Generics
Unconstrained
Types

Port element declaration syntax

```
port_element ::=
  PORT_NAME : [mode] DATA_TYPE [:= default_value]
```

- Mode
 - Possible Values: in, out, inout, buffer, linkage
 - Default (if mode is omitted): in
 - Defines the direction of a signal (can it be read, written or both)
- Example entity

```
1 entity and_gate is
2  port (
3  a : in boolean;
4  b : in boolean;
5  x : out boolean -- no semicolon here!
6 );
7 end entity;
and_gate

a

x
```



Generic element declaration syntax

generic_element ::=

GENERIC_NAME : DATA_TYPE [:= default_value]

With ports we can specify the physical interface signals of a module. However, when designing hardware oftentimes we also want to configure other design parameters that are not actual physical inputs. Consider the example of a RAM module, an important and widely used memory element in digital design. A typical design might use many RAMs with different address and data widths. It would be quite a tedious task to explicitly design RAM modules for all the different configurations one might need in a design. Moreover, an approach like this would result in a hard-to-maintain code. It would be much better to define one RAM module with parameters that select the data and address widths. This is where the generics come into play.

Generics

HWMod WS25

Ent. & Arch.
Introduction
Entities
Ports
Generics
Unconstrained
Types

Generic element declaration syntax

```
generic_element ::=
  GENERIC_NAME : DATA_TYPE [:= default_value]
```

Circuit Description with Entities and Architectures Entities Generics

■ Generic element declaration syntax generic_element ::= GENERIC_NAME : DATA_TYPE [:= default_value]
■ No mode required (all generics are "constant inputs")

As already mentioned, generics are used to parametrize entities, allowing to create modules that can be adapted to different use cases with different settings, such as sizes, delays, or other operational parameters. The declaration of generics looks very similar to a port declaration – the only difference is that no mode is needed as all generics can be viewed as constant inputs. Generics will become important when we talk about the instantiation of modules in the next lecture.

Generics

HWMod WS25

Ent. & Arch.
Introduction
Entities
Ports
Generics
Unconstrained
Types

Generic element declaration syntax

```
generic_element ::=
  GENERIC_NAME : DATA_TYPE [:= default_value]
```

■ No mode required (all generics are "constant inputs")

☐ Circuit Description with Entities and Architectures ☐ Entities ☐ Generics

- Generic element declaration syntax
 Generic element ---
 - generic_element ::=

 GENERIC_NAME : DATA_TYPE [:= default_value]

 No mode required (all generics are "nonstant inques")
 - No mode required (all generics are "consta
 Parically constants in the architecture

From the point of view of an architecture implementing an entity, generics can simply be viewed as constants, that are fixed at compile-time. Hence, even in synthesizable modules, it is possible to use non-synthesizable datatypes here. An example would be a time constant for the clock period or other timing parameters.

Generics

HWMod WS25

Ent. & Arch.
Introduction
Entities
Ports
Generics
Unconstrained
Types

Generic element declaration syntax

```
generic_element ::=
  GENERIC_NAME : DATA_TYPE [:= default_value]
```

- No mode required (all generics are "constant inputs")
- Basically constants in the architecture

Circuit Description with Entities and Architectures Entities Generics

Note that port declarations may refer to generics and use them to constrain port datatypes. This is also done in the example code shown on this slide. The entity is quite similar to the one on the previous slide. However, the two input signals have been replaced by an input vector named \pm . The width of this vector is defined by the generic N, allowing you to create AND-gates with arbitrary many inputs based on a single entity. This is a code pattern, you will encounter quite often in VHDL code.

Generics

HWMod WS25

Ent. & Arch.
Introduction
Entities
Ports
Generics
Unconstrained
Types

Generic element declaration syntax

```
generic_element ::=
  GENERIC_NAME : DATA_TYPE [:= default_value]
```

- No mode required (all generics are "constant inputs")
- Basically constants in the architecture
- Example entity

```
1 entity and_gate is
2   generic (
3          N : integer := 2
4          );
5   port (
6          i : in boolean_vector(N-1 downto 0);
7          x : out boolean
8     );
9 end entity;
```

Circuit Description with Entities and Architectures Entities Unconstrained Types



Note that it is also possible to use unconstrained types for generics and ports. For certain datatypes like strings, this is even necessary to make reasonable use of them as generics because not all possible values might have the same character length. In fact, in practice strings are sometimes used to enable or disable certain settings in an entity. The first example code shows how something like this can look like. Note how the two strings "yes" and "no", that the entity expects the generic to have, are of different length.

Unconstrained Types

HWMod WS25

Ent. & Arch.
Introduction
Entities
Ports
Generics
Unconstrained
Types

Unconstrained generic example

```
1 entity cpu is
2  generic (
3    ENABLE_BRANCH_PREDICTION : string := "YES"; -- "NO"
4    [...]
5  );
6   [...]
7 end entity;
```

Circuit Description with Entities and Architectures Entities Unconstrained Types



Unconstrained datatypes can also come in handy for port declarations. The second example shows yet another variant of the AND-gate entity. This time no generic is used and the input i is simply left unconstrained. Whenever this entity is instantiated, the width of this input signal is then implicitly constrained by the vector signal that is connected to i.

Unconstrained Types

HWMod WS25

Ent. & Arch.
Introduction
Entities
Ports
Generics
Unconstrained
Types

Unconstrained generic example

```
1 entity cpu is
2  generic (
3    ENABLE_BRANCH_PREDICTION : string := "YES"; -- "NO"
4    [...]
5  );
6  [...]
7 end entity;
```

Unconstrained port example

```
1 entity and_gate is
2  port (
3     i : in boolean_vector;
4     x : out boolean
5  );
6 end entity;
```

Now that we are familiar with how to specify module interfaces in VHDL, let's turn to architectures and see how they can be used to describe actual digital circuits. The VHDL standard defines architectures as the body of a design entity.

Architectures

HWMod WS25

Ent. & Arch.
Introduction
Entities
Architectures
Concurrent
Assignments
Signal Declarations

"An architecture body defines the body of a design entity."

Circuit Description with Entities and Architectures
Architectures
Architectures

■ VHDL standard ◆:

"An architecture body defines the body of a design entity."

■ Contains the actual circuit description

Thus, an architecture defines the internal behavior and structure of a digital design, and essentially specifies how the inputs of an entity have to be processed to create the output signals.

Architectures

HWMod WS25

Ent. & Arch.
Introduction
Entitles
Architectures
Concurrent
Assignments

- VHDL standard ♦:

 "An architecture body defines the body of a design entity."
- Contains the actual circuit description

```
Circuit Description with Entities and Architectures
Architectures
Architectures
```

```
■ VHOL standard Φ:

**An architecture body defines the body of a design entity!

**Cortains the actual cross of cortains of the cortain of t
```

An architecture is declared using the architecture keyword followed by an identifier, representing its name, the keyword of and another identifier specifying the entity this architecture belongs to.

Architectures

- HWMod WS25
- Ent. & Arch.
 Introduction
 Entitles
 Architectures
 Concurrent
 Assignments
- VHDL standard ♦:

 "An architecture body defines the body of a design entity."
- Contains the actual circuit description
- Architecture declaration syntax

```
architecture NAME of ENTITY_NAME is
  architecture_declarative_part
begin
  architecture_statement_part
end architecture;
```

-Circuit Description with Entities and Architectures Architectures Architectures

■ VHDL standard ◆: "An architecture body defines the body of a design entity. Contains the actual circuit description

Contains the actual circuit description

Architecture declaration syntax

architecture NAME of ENTITY_NAME

architecture_declarative_part eclarative/statement part

After the keyword is follow the architecture's declarative and statement part, which are separated by the begin keyword. As you can see from the syntax specification, both of these parts can contain zero or more elements. The VHDL standard refers to these elements as block declarative items and concurrent statements, respectively.

Architectures



Architectures

- "An architecture body defines the body of a design entity."
- Contains the actual circuit description
- Architecture declaration syntax

```
architecture NAME of ENTITY NAME is
  architecture declarative part
begin
  architecture_statement_part
end architecture;
```

Declarative/statement part

```
architecture_declarative_part ::=
                            { block_declarative_item }
architecture_statement_part
                              { concurrent_statement
```

Circuit Description with Entities and Architectures
Architectures
Architecture (cont'd)

Declarative part (block declarative items) «
 Signals
 Coresants
 Types
 Sub-programs
 etc.

As the name suggests, the declarative part, contains declarations for various VHDL language constructs, such as constants, signals, types, subprograms and others.

Architecture (cont'd)

HWMod WS25

Ent. & Arch.
Introduction
Entitles
Architectures
Concurrent
Assignments
Signal Declarations

- Declarative part (block declarative items) ◆
 - Signals
 - Constants
 - Types
 - Sub-programs
 - etc.

```
Circuit Description with Entities and Architectures
Architectures
Architecture (cont'd)
```

```
E Declarative part (block declarative items) ©
Signals
Constants
Types
Sub-programs
Sub-programs
Sub-programs
Sub-programs
Sub-programs
I Statement part (concurrent statements) ©
Concurrent signal assignments
I instanti
```

There are various types of concurrent statements that can go into the statements part of an architecture. In this lecture we will focus on the concurrent signal assignments. While we have already seen quite a few processes during the previous lectures, as most of the code samples were build around them, we have only used them in non-synthesizable contexts so far. We will discuss processes for synthesizable code, instantiations of entities as well as block and generate statements in upcoming lectures.

Architecture (cont'd)

HWMod WS25

- Ent. & Arch.
 Introduction
 Entities
 Architectures
 Concurrent
 Assignments
 Signal Declarations
- Declarative part (block declarative items) ◆
 - Signals
 - Constants
 - Types
 - Sub-programs
 - etc.
- Statement part (concurrent statements) ◆
 - Concurrent signal assignments
 - Processes
 - Instantiation statements
 - Blocks statements
 - Generate statements
 - etc.

Circuit Description with Entities and Architectures Architectures

-Concurrent Signal Assignments - Example: AND gate






We will now introduce concurrent signal assignments. To do that let us start with a very basic example and implement an architecture for the "AND"-gate entity we showed before using such a concurrent signal assignment. The assignment is located in line 11 of the sample code. Notice that VHDL uses a different assignment operator for signals than for variables.

Concurrent Signal Assignments - Example: AND gate

```
HWMod
WS25
```

```
Ent. & Arch.
Introduction
Entitles
Architectures
Concurrent
Assignments
Signal Declarations
```
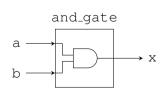
```
1 entity and_gate is
2 port (
3    a : in boolean;
4    b : in boolean;
5    x : out boolean
6  );
7 end entity;
8
9 architecture arch of and_gate is
10 begin
11    x <= a and b;
12 end architecture;</pre>
```



—Circuit Description with Entities and Architectures ☐Architectures

-Concurrent Signal Assignments - Example: Multiplexer




Let's look at a slightly more complex example, that of a four-to-one multiplexer. As you should already know, the function of a multiplexer is to relay one of the inputs to a single output based on the value of a control input. In our case here, we want to multiplex between four input signals $\pm (0)$ to ± 3 , for which we need to control inputs $\pm (0)$ and $\pm (1)$. To implement the multiplexer we use a so-called conditional signal assignment. Essentially, this is a compact way to specify an if-else-if construct in a single expression. You can compare it to a nested ternary conditional operator in other programming languages such as Java or C. If both control signals are false then the output gets assigned the input $\pm (0)$. If only $\pm (0)$ is true, $\pm (1)$ is selected, and so on. The right side of the slide depicts the circuit symbol that we will use for multiplexers throughout this course.

Concurrent Signal Assignments – Example: Multiplexer

HWMod WS25

Ent. & Arch.
Introduction
Entities
Architectures
Concurrent
Assignments

```
1 entity mux41 is
   port (
    c : in boolean_vector(1 downto 0);
    i : in boolean vector(3 downto 0);
    o : out boolean
   );
7 end entity;
9 architecture arch of mux41 is
10 begin
   o \le i(0) when not c(1) and not c(0) else
         i(1) when not c(1) and
                                     c(0) else
12
13
         i(2) when
                       c(1) and not c(0) else
         i(3) when
                       c(1) and
                                     c(0);
14
15 end architecture;
```

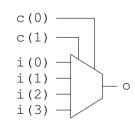

Circuit Description with Entities and Architectures
Architectures
Signal Declarations

Signal declaration syntax signal NAME: DATA_TYPE [:= default_value];

It is of course also possible to declare local signals in an architecture that are not visible to the outside world. As you might have suspected, such declaration go into the declarative part of the architecture. The syntax for that is quite straight-forward and basically looks very similar to a variable or constant declaration that we have already seen multiple times. However, before we further elaborate, it is important to discuss a detail that we more or less glossed over so far.

Signal Declarations



Ent. & Arch.
Introduction
Entitles
Architectures
Concurrent
Assignments
Signal Declarations

Signal declaration syntax

```
signal NAME : DATA_TYPE [ := default_value ] ;
```

Circuit Description with Entities and Architectures Architectures Signal Declarations

Signal declaration syntax
signal subset : DATA_TYPE [:= default_value] ;

Signals vs. variables
Signals
Uariables
Declaration: (as) ports. enfiles, arribterbuse newhouse.

Declaration: subprograms, arribterbuse newhouse.

In VHDL there is a fundamental difference between objects of type signal – that also includes the ports declared in an entity – and variables. Signals represent and model physical connections between hardware components such as gates or registers. They can be declared in the declarative part of architectures or entities as well as in packages. Furthermore, some architecture statements such as blocks or generate statements can have their own local signals. However, they cannot be declared in subprograms or processes. Here only variable declarations are allowed, representing local values that are only relevant during the evaluation of a process or a subprogram. The major difference comes from the way these two classes of objects are treated during simulation and synthesis. In strongly simplified terms: Signal assignment affect the internal event queue the simulator has to maintain, whereas variable assignments do not and are executed immediately. As we have already seen VHDL even goes so far as to use unique assignment operators for signals and variables, to also highlight this difference syntactically. However, we don't want to go into too much detail here – as this is the content of another lecture.

Signal Declarations

HWMod WS25

Ent. & Arch.
Introduction
Entities
Architectures
Concurrent
Assignments
Signal Declarations

Signal declaration syntax

signal NAME : DATA_TYPE [:= default_value] ;

Signals vs. variables

Signals

- Declaration: (as) ports, entities, architectures, packages
- Assignment: deferred (event queue)
- Assignment operator: <=</p>

Variables

- Declaration: subprograms, processes
- Assignment: immediate
- Assignment operator: :=

Circuit Description with Entities and Architectures Architectures Example - Full Adder






Let's look at a slightly more complex example that uses local signal declarations. A full adder, such as the one shown on the left side of the slide, is a digital circuit with three inputs -a, b, and cin-and two outputs -sum and cout. Its purpose is to add the three single-bit input signals and produce a 2-bit result consisting of the sum bit and a carry output. In order to add multi-bit signals, multiple full adders can be connected together in the form of a ripple-carry adder.

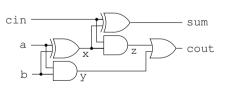Example - Full Adder

HWMod WS25

Ent. & Arch.
Introduction
Entities
Architectures
Concurrent
Assignments
Signal Declarations



```
1 entity fa is
2 port (
3 a, b, cin : in boolean;
4 sum, cout : out boolean
5 );
6 end entity;
```

☐ Circuit Description with Entities and Architectures ☐ Architectures ☐ Example - Full Adder




To implement the circuit the example uses three intermediate signals named "x", "y" and "z". You can see which circuit nodes these signals represent in the schematic on the left. The five concurrent signal assignments correspond to the five gates in the circuit and should be quite straight-forward to understand. However, you can pause the video to convince yourself that this is indeed the case.

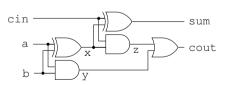Example - Full Adder

HWMod WS25

Ent. & Arch.
Introduction
Entitles
Architectures
Concurrent
Assignments
Signal Declarations



```
1 entity fa is
2 port (
3 a, b, cin : in boolean;
4 sum, cout : out boolean
5 );
6 end entity;
7
8 architecture arch of fa is
9 signal x, y, z : boolean;
10 begin
11 x <= a xor b;
12 y <= a and b;
13 sum <= cin xor x;
14 z <= cin and x;
15 cout <= y or z;
16 end architecture;</pre>
```

☐ Circuit Description with Entities and Architectures ☐ Architectures ☐ Example - Full Adder




One key take-away from this code is that the sequence of the assignment statements does not matter in any way. No matter how you arrange the statements in an architecture the semantic of the architecture stays the same. Unlike in software, where statements are executed strictly in sequence, in a circuit a lot of things happen in parallel. The individual gates in a circuit always evaluate their inputs and produce a new output signal level. Hence, you can think of the individual statements in an architecture as individual threads that are all executed in parallel. This is the reason why they are called "concurrent" signal assignments. This is a key insight that will be very important throughout this course and your journey with VHDL.

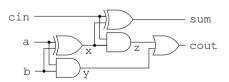Example - Full Adder

HWMod WS25

Ent. & Arch.
Introduction
Entitles
Architectures
Concurrent
Assignments
Signal Declarations



Important

The order of statements in an architecture carries **no** semantic significance!

```
1 entity fa is
2 port (
3   a, b, cin : in boolean;
4   sum, cout : out boolean
5 );
6 end entity;
7
8 architecture arch of fa is
9 signal x, y, z : boolean;
10 begin
11 x <= a xor b;
12 y <= a and b;
13 sum <= cin xor x;
14 z <= cin and x;
15 cout <= y or z;
16 end architecture;</pre>
```

Thank you for listening! We recommend you to immediately take the self-check test in TUWEL, to see if you understood the material presented in this lecture.



Introduction
Entities
Architectures
Concurrent
Assignments
Signal Declarations

Lecture Complete!