

Hardware Modeling [VU] (191.011)

– WS25 –

Finite-State Machine Basics

Florian Huemer & Sebastian Wiedemann & Dylan Baumann

WS 2025/26

Introduction

HWMod
WS25

FSM Basics

Introduction

FSM Circuits

Example: Timer

- Fundamental structure in digital designs

Introduction

HWMod
WS25

FSM Basics
Introduction
FSM Circuits
Example: Timer

- Fundamental structure in digital designs
- An FSM consists of a
 - set of inputs, outputs and states
 - transition function

Introduction

HWMod
WS25

FSM Basics
Introduction
FSM Circuits
Example: Timer

- Fundamental structure in digital designs
- An FSM consists of a
 - set of inputs, outputs and states
 - transition function
- Synchronous FSMs: State changes **only** happen at clock events!

Introduction

HWMod
WS25

FSM Basics
Introduction
FSM Circuits
Example: Timer

- Fundamental structure in digital designs
- An FSM consists of a
 - set of inputs, outputs and states
 - transition function
- Synchronous FSMs: State changes **only** happen at clock events!
- Important VHDL concepts used in the lecture
 - Enumeration and record types
 - Behavioral modeling of combinational logic
 - Sequential circuit elements (i.e., registers)

State Machine as Digital Circuits

HWMod
WS25

FSM Basics

Introduction


FSM Circuits

Next-State Logic

State Register

Output Logic

Example: Timer

 

Next-State Logic

HWMod
WS25

FSM Basics

Introduction

FSM Circuits


Next-State Logic

State Register

Output Logic

 Example: Timer

- Purely combinational
 - **Must not** read the clock or reset
 - **Must not** contain latches



Next-State Logic

HWMod
WS25

FSM Basics

Introduction

FSM Circuits


Next-State Logic

State Register

Output Logic

 Example: Timer

- Purely combinational
 - **Must not** read the clock or reset
 - **Must not** contain latches
- Implements the transition function
 - by reading the **input** and the **current state**
 - to calculate the **next state** of the FSM



Next-State Logic

HWMod
WS25

FSM Basics

Introduction

FSM Circuits



Next-State Logic

State Register

Output Logic

  Example: Timer

- Purely combinational
 - **Must not** read the clock or reset
 - **Must not** contain latches
- Implements the transition function
 - by reading the **input** and the **current state**
 - to calculate the **next state** of the FSM
- State changes are synchronous!



State Register

HWMod
WS25

FSM Basics

Introduction


FSM Circuits

Next-State Logic

State Register

Output Logic

Example: Timer

 

- Only synchronous component in the FSM
- Reads **next state** and outputs **current state**

State Register

HWMod
WS25

FSM Basics

Introduction


FSM Circuits

Next-State Logic

State Register

Output Logic

Example: Timer

 

- Only synchronous component in the FSM
- Reads **next state** and outputs **current state**
- **Strictly** stick to the code patterns for registers!

State Register

HWMod
WS25

FSM Basics

Introduction


FSM Circuits

Next-State Logic

State Register

Output Logic

Example: Timer

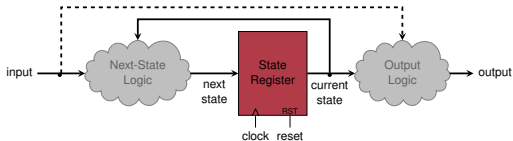

- Only synchronous component in the FSM
- Reads **next state** and outputs **current state**
- **Strictly** stick to the code patterns for registers!
- Reset value defines initial state

Output Logic

HWMod
WS25

FSM Basics

Introduction

FSM Circuits


Next-State Logic

State Register

Output Logic

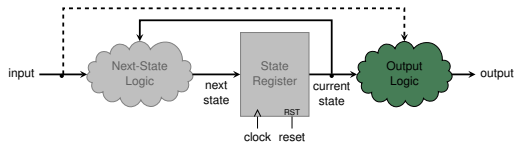Example: Timer

- Purely combinational
 - **Must not** read the clock or reset
 - **Must not** contain latches



Output Logic

HWMod
WS25

FSM Basics

Introduction

FSM Circuits


Next-State Logic

State Register

Output Logic

 Example: Timer

- Purely combinational
 - **Must not** read the clock or reset
 - **Must not** contain latches
- Produces the actual **output** signals



Output Logic

HWMod
WS25

FSM Basics

Introduction

FSM Circuits


Next-State Logic

State Register

Output Logic

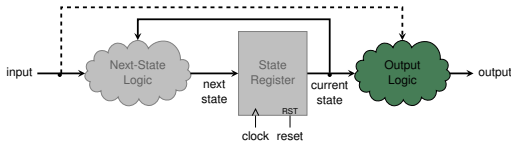Example: Timer

- Purely combinational
 - **Must not** read the clock or reset
 - **Must not** contain latches
- Produces the actual **output** signals
- Defines the FSM type
 - Moore: Output depends solely on **current state**
 - Mealy: Output depends on **current state** and **input**



Output Logic

HWMod
WS25

FSM Basics

Introduction

FSM Circuits


Next-State Logic

State Register

Output Logic

 Example: Timer

- Purely combinational
 - **Must not** read the clock or reset
 - **Must not** contain latches
- Produces the actual **output** signals
- Defines the FSM type
 - Moore: Output depends solely on **current state**
 - Mealy: Output depends on **current state** and **input**
- Mealy machines
 - can react to input changes in the **same** clock cycle (i.e., combinational)
 - (sometimes) require fewer states than a similar Moore machine



Output Logic

HWMod
WS25

FSM Basics

Introduction

FSM Circuits


Next-State Logic

State Register

Output Logic

 Example: Timer

- Purely combinational
 - **Must not** read the clock or reset
 - **Must not** contain latches
- Produces the actual **output** signals
- Defines the FSM type
 - Moore: Output depends solely on **current state**
 - Mealy: Output depends on **current state** and **input**
- Mealy machines
 - can react to input changes in the **same** clock cycle (i.e., combinational)
 - (sometimes) require fewer states than a similar Moore machine
- Can share logic with the next-state logic



Output Logic - Combinational Loops

HWMod
WS25

FSM Basics

Introduction

FSM Circuits

Next-State Logic

State Register

Output Logic

Example: Timer

- Interacting Mealy FSMs can lead to combinational loops!

Output Logic - Combinational Loops

HWMod
WS25

FSM Basics

Introduction

FSM Circuits


Next-State Logic

State Register

Output Logic

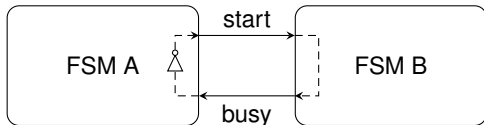Example: Timer

- Interacting Mealy FSMs can lead to combinational loops!
- Example
 - FSM A: “Start when not busy”
 - FSM B: “Assert busy when started”



Output Logic - Combinational Loops

HWMod
WS25

FSM Basics

Introduction

FSM Circuits


Next-State Logic

State Register

Output Logic

 Example: Timer

- Interacting Mealy FSMs can lead to combinational loops!
- Example
 - FSM A: “Start when not busy”
 - FSM B: “Assert busy when started”



- Only use Mealy machines when **really** necessary

Simple Timer - Specification

HWMod
WS25

FSM Basics

Introduction

FSM Circuits

Example: Timer

Specification

Circuit

Implementation

Behavior Description

The `simple_timer` module keeps an internal N -bit counter that is (synchronously) incremented as long as `en` is asserted. When the counter reaches its maximum value ($2^N - 1$) it overflows back to zero. If the counter hits its maximum and `en` is asserted the `tick` output is asserted.

Interface


```
1 entity simple_timer is
2   generic (
3     N : positive := 8
4   );
5   port (
6     clk    : in std_ulogic;
7     res_n  : in std_ulogic;
8     en     : in std_ulogic;
9     tick   : out std_ulogic
10  );
11 end entity;
```

Simple Timer - Circuit

HWMod
WS25

FSM Basics

 - Introduction
- FSM Circuits
- Example: Timer
- Specification
- Circuit
- Implementation




Simple Timer - Circuit

HWMod
WS25

FSM Basics

 - Introduction
- FSM Circuits
- Example: Timer
- Specification
- Circuit
- Implementation



Simple Timer - Implementation

HWMod
WS25

FSM Basics

Introduction


FSM Circuits

Example: Timer

Specification

Circuit

Implementation

 

```
1 architecture arch of simple_timer is
2     subtype cnt_t is
3         unsigned(N-1 downto 0);
4     signal cnt, cnt_nxt : cnt_t;
5     constant M : natural := 2**N-1;
6 begin
7
8     state_reg : process(clk, res_n)
9     begin
10        if res_n = '0' then
11            cnt <= (others => '0');
12        elsif rising_edge(clk) then
13            cnt <= cnt_nxt;
14        end if;
15    end process;
16
17    next_state_logic : process(all)
18    begin
19        cnt_nxt <= cnt;
20        if en = '1' then
21            cnt_nxt <= cnt + 1;
22        end if;
23    end process;
24
25    output_logic : process(all)
26    begin
27        variable comp : std_ulogic;
28        comp := '1' when cnt=M else '0';
29        tick <= en and comp;
30    end process;
31 end architecture;
```


Simple Timer - Implementation

HWMod
WS25

FSM Basics

Introduction


FSM Circuits

Example: Timer

Specification

Circuit

Implementation

 

```
1 architecture arch of simple_timer is
2     subtype cnt_t is
3         unsigned(N-1 downto 0);
4     signal cnt, cnt_nxt : cnt_t;
5     constant M : natural := 2**N-1;
6 begin
7
8     state_reg : process(clk, res_n)
9     begin
10         if res_n = '0' then
11             cnt <= (others => '0');
12         elsif rising_edge(clk) then
13             cnt <= cnt_nxt;
14         end if;
15     end process;
16
17     next_state_logic : process(all)
18     begin
19         cnt_nxt <= cnt;
20         if en = '1' then
21             cnt_nxt <= cnt + 1;
22         end if;
23     end process;
24
25     output_logic : process(all)
26     variable comp : std_ulogic;
27     begin
28         comp := '1' when cnt=M else '0';
29         tick <= en and comp;
30     end process;
31 end architecture;
```

Simple Timer - Implementation

HWMod
WS25

FSM Basics

Introduction


FSM Circuits

Example: Timer

Specification

Circuit

Implementation

 

```
1 architecture arch of simple_timer is
2     subtype cnt_t is
3         unsigned(N-1 downto 0);
4     signal cnt, cnt_nxt : cnt_t;
5     constant M : natural := 2**N-1;
6 begin
7
8     state_reg : process(clk, res_n)
9     begin
10         if res_n = '0' then
11             cnt <= (others => '0');
12         elsif rising_edge(clk) then
13             cnt <= cnt_nxt;
14         end if;
15     end process;
16
17     next_state_logic : process(all)
18     begin
19         cnt_nxt <= cnt;
20         if en = '1' then
21             cnt_nxt <= cnt + 1;
22         end if;
23     end process;
24
25     output_logic : process(all)
26     begin
27         variable comp : std_ulogic;
28         comp := '1' when cnt=M else '0';
29         tick <= en and comp;
30     end process;
31 end architecture;
```

Simple Timer - Implementation

HWMod
WS25

FSM Basics

Introduction


FSM Circuits

Example: Timer

Specification

Circuit

Implementation

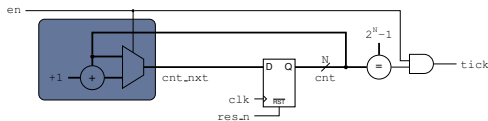

```

1 architecture arch of simple_timer is
2     subtype cnt_t is
3         unsigned(N-1 downto 0);
4     signal cnt, cnt_nxt : cnt_t;
5     constant M : natural := 2**N-1;
6 begin
7
8     state_reg : process(clk, res_n)
9     begin
10         if res_n = '0' then
11             cnt <= (others => '0');
12         elsif rising_edge(clk) then
13             cnt <= cnt_nxt;
14         end if;
15     end process;

```

```

16 next_state_logic : process(all)
17 begin
18     cnt_nxt <= cnt;
19     if en = '1' then
20         cnt_nxt <= cnt + 1;
21     end if;
22 end process;
23
24 output_logic : process(all)
25     variable comp : std_ulogic;
26 begin
27     comp := '1' when cnt=M else '0';
28     tick <= en and comp;
29 end process;
30 end architecture;

```

Simple Timer - Implementation

HWMod
WS25

FSM Basics

Introduction


FSM Circuits

Example: Timer

Specification

Circuit

Implementation

 

```

1 architecture arch of simple_timer is
2     subtype cnt_t is
3         unsigned(N-1 downto 0);
4     signal cnt, cnt_nxt : cnt_t;
5     constant M : natural := 2**N-1;
6 begin
7
8     state_reg : process(clk, res_n)
9     begin
10         if res_n = '0' then
11             cnt <= (others => '0');
12         elsif rising_edge(clk) then
13             cnt <= cnt_nxt;
14         end if;
15     end process;
16
17     next_state_logic : process(all)
18     begin
19         cnt_nxt <= cnt;
20         if en = '1' then
21             cnt_nxt <= cnt + 1;
22         end if;
23     end process;
24
25     output_logic : process(all)
26     begin
27         variable comp : std_ulogic;
28         comp := '1' when cnt=M else '0';
29         tick <= en and comp;
30     end process;
31 end architecture;

```

Simple Timer - Implementation

HWMod
WS25

FSM Basics

Introduction


FSM Circuits

Example: Timer

Specification

Circuit

Implementation

 

```
1 architecture arch of simple_timer is
2     subtype cnt_t is
3         unsigned(N-1 downto 0);
4     signal cnt, cnt_nxt : cnt_t;
5     constant M : natural := 2**N-1;
6 begin
7
8     state_reg : process(clk, res_n)
9     begin
10         if res_n = '0' then
11             cnt <= (others => '0');
12         elsif rising_edge(clk) then
13             cnt <= cnt_nxt;
14         end if;
15     end process;
16
17     next_state_logic : process(all)
18     begin
19         cnt_nxt <= cnt;
20         if en = '1' then
21             cnt_nxt <= cnt + 1;
22         end if;
23     end process;
24
25     output_logic : process(all)
26     begin
27         variable comp : std_ulogic;
28         comp := '1' when cnt=M else '0';
29         tick <= en and comp;
30     end process;
31 end architecture;
```

Lecture Complete!