

Hardware Modeling [VU] (191.011)

– WS25 –

Finite-State Machine Implementation (in VHDL)

Florian Huemer & Sebastian Wiedemann & Dylan Baumann

WS 2025/26

Implementing FSMs in VHDL

HWMod
WS25

FSM Imple-
mentation
Implementation
Steps
Example

- Conversion of FSM model to VHDL code follows simple steps
 - 1 Create an enumeration type for the FSM state
 - 2 Create a record type for the state register
 - 3 Create signals for the current (`s`) and next (`s_next`) register value
 - 4 Implement the state register in a sync. process
 - 5 Implement the next-state and output logic in comb. process(es)
- 2- vs. 3-process method
 - Overlap of next-state and output logic $\Rightarrow$ 2-process usually more readable
 - Recommendation: Use the 2-process method

Example: FSM Types

HWMod
WS25

- 1 Create an enumeration type for the FSM state
- 2 Create a record type for the state register

FSM Imple-
mentation


Implementation
Steps

Example

FSM Types

State Register

Comb. Logic

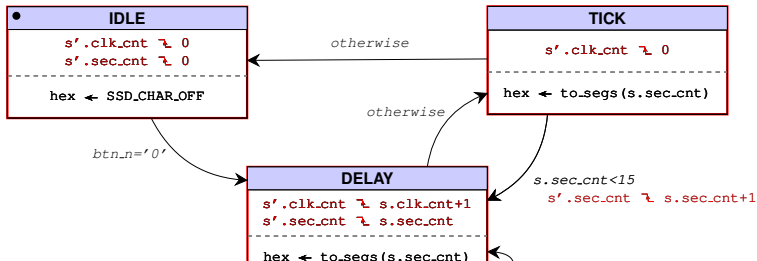


Example: State Register

HWMod
WS25

3 Create signals for the current (s) and next (s_nxt) register value

4 Implement the state register in a sync. process
 
```
18 architecture arch of advanced_timer is
19   -- enum and record declarations
```



FSM Imple-
mentation

Implementation
Steps

Example

FSM Types

State Register

Comb. Logic

Example: Next-State and Output Logic

HWMod
WS25

FSM Imple-
mentation

Implementation
Steps

Example


FSM Types

State Register

Comb. Logic

- 5 Implement the next-state and output logic in comb. process
- **Recall:** Path without assignment through comb. process $\Rightarrow$ latch!
- $\Rightarrow$ Recommendation: Use default assignments
- Define next-state and output logic per state
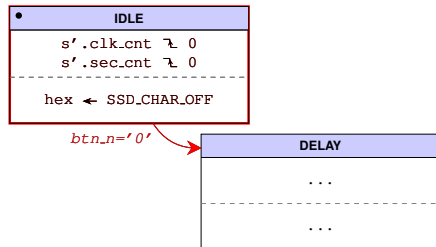
```
36 comb : process(all)
37 begin
38     s_nxt <= s;
39     hex <= to_segs(std_ulogic_vector(s.tick_cnt));
```



Example: Next-State and Output Logic (cont'd)

HWMoD
WS25

FSM Imple-
mentation

Implementation
Steps


Example

FSM Types

State Register

Comb. Logic

```
36 comb : process(all)
37 begin
38     s_nxt <= s;
39     hex <= to_segs(std_ulogic_vector(s.tick_cnt));
40
41     case s.state is
42         when IDLE =>
43             s_nxt.clk_cnt <= (others => '0');
44             s_nxt.tick_cnt <= (others => '0');
45             hex <= SSD_CHAR_OFF;
46             if btn_n = '0' then
47                 s_nxt.state <= DELAY;
48             end if;
49
50         when DELAY =>
51             if s.clk_cnt < CLK_FREQ-1 then
52                 s_nxt.clk_cnt <= s.clk_cnt + 1;
53             else
54                 s_nxt.state <= TICK;
55             end if;
56         when TICK =>
57             s_nxt.clk_cnt <= (others => '0');
58             s_nxt.state <= DELAY;
59             if s.tick_cnt < 15 then
60                 s_nxt.tick_cnt <= s.tick_cnt + 1;
61             else
62                 s_nxt.state <= IDLE;
63             end if;
```

 

Lecture Complete!