

Hardware Modeling [VU] (191.011)

– WS25 –

Latches and combinational loops

Florian Huemer & Sebastian Wiedemann & Dylan Baumann


WS 2025/26

Undesired Latches

HWMod
WS25

Latches &
Loops
Latches
Comb. Loops
Summary

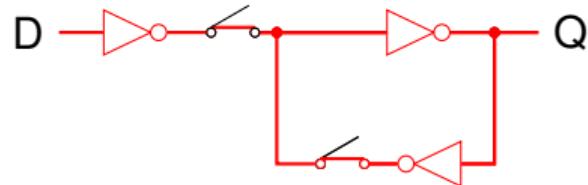- When should you use a latch or a flip-flop?
- In this course latches are **always** undesired
- Often not available as primitive building blocks
 - Built from combinational elements instead
 - Delay of feedback path can become high
 - Feedback path can lead to oscillation




Pitfalls - Latch Errors (cont'd)

HWMod
WS25

Latches &
Loops
Latches
Comb. Loops
Summary

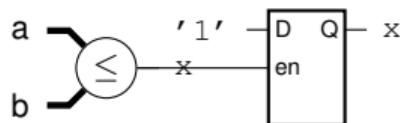- How do latches *happen*?
 - Not all paths write to signal
 - Holding state \Rightarrow infer latch
- Always cover all paths/cases!
 - Default assignment or `others`
- Detected during synthesis
 - **Never** ignore warnings!




```
1 entity cmp is
2   port(
3     a, b : in  unsigned;
4     x    : out std_ulogic
5   );
6 end entity;
7
8 architecture arch of cmp is
9 begin
10  main : process (all) begin
11
12    if a <= b then
13      x <= '1';
14    end if;
15  end process;
16 end architecture;
```

Pitfalls - Combinational Loops

HWMod
WS25

Latches &
Loops
Latches
Comb. Loops
Summary

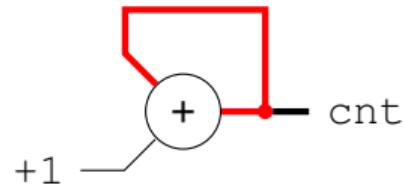- Feedback loops not exclusive to latches
- Comb. process must never read **and** write to same signal
 - Hard to spot at interfaces
 - Feedback paths must contain flip-flops
- Also reported during synthesis




Pitfalls - Combinational Loops (cnt'd)

HWMod
WS25

Latches &
Loops
Latches
Comb. Loops
Summary
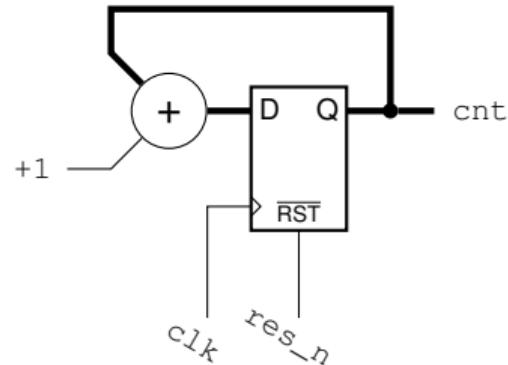
```
1 architecture sync of counter is
2   signal cnt, cnt_next : unsigned(7 downto 0);
3 begin
4
5
6
7
8
9
10
11
12
13
14
15 end architecture;
```



Summary

HWMod
WS25

Latches &
Loops
Latches
Comb. Loops
Summary

- Latches
 - Often due to missing default values
- Comb. loops
 - Never read **and** write same signal
 - Never ignore tool warnings!

10631 VHDL Process Statement warning at top_arch.vhd(13): inferring latch(es) for signal or variable "abc", which holds its previous value in one or more paths through the process

332125 Found combinational loop of 2 nodes

Lecture Complete!