

Hardware Modeling [VU] (191.011)

– WS25 –

Sequential Circuit Example: LFSR

Florian Huemer & Sebastian Wiedemann & Dylan Baumann


WS 2025/26

Example: 4-bit LFSR

HWMod
WS25

LFSR

Operation
VHDL Design
Testbench

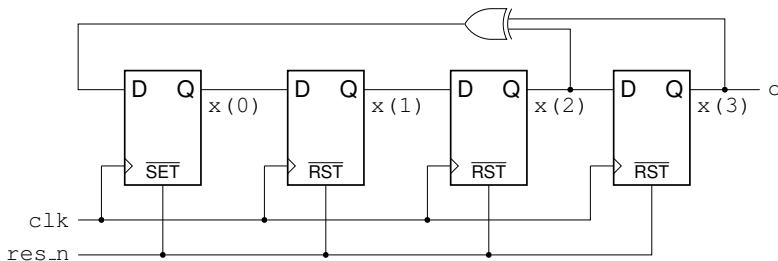

- **Linear Feedback Shift Register**
- Chain of FFs (*shift-register*) fed by linear combination of its current state
- Pseudo-random sequence of bits

LFSR - Circuit Operation Principle


HWMod
WS25

LFSR

Operation

VHDL Design

Testbench

 


LFSR - VHDL Design

HWMod
WS25

LFSR

Operation
VHDL Design
Testbench

 

```
1 entity lfsr is
2   port (
3     clk    : in  std_ulogic;
4     res_n  : in  std_ulogic;
5     o      : out std_ulogic
6   );
7 end entity;
```

```
9 architecture arch of lfsr is
10   signal x : std_ulogic_vector(0 to 3);
11 begin
12
13
14
15
16
17
18
19
20
21
22
23
24 end architecture;
```

LFSR - Testbench

HWMod
WS25

LFSR

Operation
VHDL Design
Testbench

```
1 architecture bench of lfsr_tb is
2   signal clk : std_ulogic;
3   signal res_n : std_ulogic;
4   signal o : std_ulogic;
5
6
7
8 begin
9
10  uut : entity work.lfsr
11  port map (
12    clk => clk,
13    res_n => res_n,
14    o => o
15  );
```

```
1  clkgen : process
2  begin
3    while not stop_clk loop
4      clk <= '0';
5      wait for 0.5*CLK_PERIOD;
6      clk <= '1';
7      wait for 0.5*CLK_PERIOD;
8    end loop;
9    wait;
10 end process;
```

Lecture Complete!