

This lecture gives an introduction on RAM in digital design with a special focus on FPGAs. We will discuss how memory looks like in VHDL and how to interface with it.

HWMod
WS25

RAM

Introduction
FPGA Memory
Simple DP RAM
True DP RAM
Dual-Clocked RAM
Implementation

Hardware Modeling [VU] (191.011) – WS25 – RAM in VHDL (for FPGAs)

Florian Huemer & Sebastian Wiedemann & Dylan Baumann

WS 2025/26

RAM, or Random Access Memory, is an essential component in digital design, playing a key role in storing and accessing data efficiently. This lecture is about on-chip RAM, that is, memory integrated within the design itself – in the case of this course, this means inside the FPGA.

Introduction

- On-chip RAM is a fundamental building block in digital design

HWMoD
WS25

RAM
Introduction
FPGA Memory
Simple DP RAM
True DP RAM
Dual-Clocked RAM
Implementation

On-chip RAM provides fast and flexible data storage capabilities directly on silicon, which is crucial for applications requiring high-speed data processing and low-latency access, as it minimizes the delay associated with external memory communication.

Introduction

- On-chip RAM is a fundamental building block in digital design
- Fast, low-latency, flexible data storage

HWMoD
WS25

RAM
Introduction
FPGA Memory
Simple DP RAM
True DP RAM
Dual-Clocked RAM
Implementation

So far, in this course, we have only covered flip-flops and latches as storage elements. Compared to these components, RAM offers several advantages and trade-offs.

Introduction

HWMoD
WS25

RAM

Introduction

FPGA Memory

Simple DP RAM

True DP RAM

Dual-Clocked RAM

Implementation

- On-chip RAM is a fundamental building block in digital design
- Fast, low-latency, flexible data storage
- Compared to flip-flops/latches, RAM ...

RAM uses an address-based access mechanism. This means that, in order to access specific data in the memory, an address has to be provided. The RAM decodes this address and selects the corresponding location in its memory-array for reading or writing data. This is in contrast to latches or flip-flops where data is accessed directly without address decoding, as each flip-flop is hardwired to specific parts of a circuit.

Introduction

HWMoD
WS25

RAM

Introduction

FPGA Memory

Simple DP RAM

True DP RAM

Dual-Clocked RAM

Implementation

- On-chip RAM is a fundamental building block in digital design
- Fast, low-latency, flexible data storage
- Compared to flip-flops/latches, RAM ...
 - uses an address-based access scheme

- On-chip RAM is a fundamental building block in digital design
- Fast, low-latency, flexible data storage
- Compared to flip-flops/latches, RAM ...
 - uses an address-based access scheme
 - is more compact in terms of area and, hence, more power efficient

This approach allows RAM to be significantly more compact, leading to improved area efficiency and reduced power consumption.

Introduction

HWMoD
WS25

RAM

Introduction
FPGA Memory
Simple DP RAM
True DP RAM
Dual-Clocked RAM
Implementation

- On-chip RAM is a fundamental building block in digital design
- Fast, low-latency, flexible data storage
- Compared to flip-flops/latches, RAM ...
 - uses an address-based access scheme
 - is more compact in terms of area and, hence, more power efficient

- On-chip RAM is a fundamental building block in digital design
- Fast, low-latency, flexible data storage
- Compared to flip-flops/latches, RAM ...
 - uses an address-based access scheme
 - is more compact in terms of area and, hence, more power efficient
 - allows for higher-capacity memory
 - is slightly slower

Additionally, RAM can accommodate much larger memory capacities compared to flip-flops or latches, albeit with a trade-off in access speed, as RAM tends to be slightly slower.

Introduction

HWMoD
WS25

RAM

Introduction

FPGA Memory

Simple DP RAM

True DP RAM

Dual-Clocked RAM

Implementation

- On-chip RAM is a fundamental building block in digital design
- Fast, low-latency, flexible data storage
- Compared to flip-flops/latches, RAM ...
 - uses an address-based access scheme
 - is more compact in terms of area and, hence, more power efficient
 - allows for higher-capacity memory
 - is slightly slower

- On-chip RAM is a fundamental building block in digital design
- Fast, low-latency, flexible data storage
- Compared to flip-flops/latches, RAM ...
 - uses an address-based access scheme
 - is more compact in terms of area and, hence, more power efficient
 - allows for higher-capacity memory
 - is slightly slower
- Where do we need RAM in a design?

On-chip RAM is indispensable in a wide range of design scenarios.

Introduction

HWMoD
WS25

RAM
Introduction
FPGA Memory
Simple DP RAM
True DP RAM
Dual-Clocked RAM
Implementation

- On-chip RAM is a fundamental building block in digital design
- Fast, low-latency, flexible data storage
- Compared to flip-flops/latches, RAM ...
 - uses an address-based access scheme
 - is more compact in terms of area and, hence, more power efficient
 - allows for higher-capacity memory
 - is slightly slower
- Where do we need RAM in a design?

- On-chip RAM is a fundamental building block in digital design
- Fast, low-latency, flexible data storage
- Compared to flip-flops/latches, RAM ...
 - uses an address-based access scheme
 - is more compact in terms of area and, hence, more power efficient
 - allows for higher-capacity memory
 - is slightly slower
- Where do we need RAM in a design?
 - Buffers inside or in between modules (often in the form of FIFO buffers)

For instance, it is commonly employed as buffers within or between modules, frequently implemented as First In, First Out buffers to manage data flow.

Introduction

HWMoD
WS25

RAM

Introduction
FPGA Memory
Simple DP RAM
True DP RAM
Dual-Clocked RAM
Implementation

- On-chip RAM is a fundamental building block in digital design
- Fast, low-latency, flexible data storage
- Compared to flip-flops/latches, RAM ...
 - uses an address-based access scheme
 - is more compact in terms of area and, hence, more power efficient
 - allows for higher-capacity memory
 - is slightly slower
- Where do we need RAM in a design?
 - Buffers inside or in between modules (often in the form of FIFO buffers)

- On-chip RAM is a fundamental building block in digital design
- Fast, low-latency, flexible data storage
- Compared to flip-flops/latches, RAM ...
 - uses an address-based access scheme
 - is more compact in terms of area and, hence, more power efficient
 - allows for higher-capacity memory
 - is slightly slower
- Where do we need RAM in a design?
 - Buffers inside or in between modules (often in the form of FIFO buffers)
 - Caches for frequently accessed data in some external memory

RAM also serves as caches, which store frequently accessed data to reduce access times for external memory.

Introduction

HWMoD
WS25

RAM

Introduction
FPGA Memory
Simple DP RAM
True DP RAM
Dual-Clocked RAM
Implementation

- On-chip RAM is a fundamental building block in digital design
- Fast, low-latency, flexible data storage
- Compared to flip-flops/latches, RAM ...
 - uses an address-based access scheme
 - is more compact in terms of area and, hence, more power efficient
 - allows for higher-capacity memory
 - is slightly slower
- Where do we need RAM in a design?
 - Buffers inside or in between modules (often in the form of FIFO buffers)
 - Caches for frequently accessed data in some external memory

- On-chip RAM is a fundamental building block in digital design
- Fast, low-latency, flexible data storage
- Compared to flip-flops/latches, RAM ...
 - uses an address-based access scheme
 - is more compact in terms of area and, hence, more power efficient
 - allows for higher-capacity memory
 - is slightly slower
- Where do we need RAM in a design?
 - Buffers inside or in between modules (often in the form of FIFO buffers)
 - Caches for frequently accessed data in some external memory
 - Large look-up tables

Another critical application of RAM is in large look-up tables, enabling rapid access to precomputed values or data mappings.

Introduction

HWMoD
WS25

RAM

Introduction
FPGA Memory
Simple DP RAM
True DP RAM
Dual-Clocked RAM
Implementation

- On-chip RAM is a fundamental building block in digital design
- Fast, low-latency, flexible data storage
- Compared to flip-flops/latches, RAM ...
 - uses an address-based access scheme
 - is more compact in terms of area and, hence, more power efficient
 - allows for higher-capacity memory
 - is slightly slower
- Where do we need RAM in a design?
 - Buffers inside or in between modules (often in the form of FIFO buffers)
 - Caches for frequently accessed data in some external memory
 - Large look-up tables

- On-chip RAM is a fundamental building block in digital design
- Fast, low-latency, flexible data storage
- Compared to flip-flops/latches, RAM ...
 - uses an address-based access scheme
 - is more compact in terms of area and, hence, more power efficient
 - allows for higher-capacity memory
 - is slightly slower
- Where do we need RAM in a design?
 - Buffers inside or in between modules (often in the form of FIFO buffers)
 - Caches for frequently accessed data in some external memory
 - Large look-up tables
 - Program and data memory for processors to store instructions and data

Furthermore, processors may rely on on-chip RAM for program and data memory, storing instructions and data necessary for their operation.

Introduction

HWMoD
WS25

RAM

Introduction
FPGA Memory
Simple DP RAM
True DP RAM
Dual-Clocked RAM
Implementation

- On-chip RAM is a fundamental building block in digital design
- Fast, low-latency, flexible data storage
- Compared to flip-flops/latches, RAM ...
 - uses an address-based access scheme
 - is more compact in terms of area and, hence, more power efficient
 - allows for higher-capacity memory
 - is slightly slower
- Where do we need RAM in a design?
 - Buffers inside or in between modules (often in the form of FIFO buffers)
 - Caches for frequently accessed data in some external memory
 - Large look-up tables
 - Program and data memory for processors to store instructions and data

A key characteristic of RAM is its capacity, which is determined by two factors: the data width and the depth.

Introduction (cont'd)

- RAM capacity (C)

HWMoD
WS25

RAM
Introduction
FPGA Memory
Simple DP RAM
True DP RAM
Dual-Clocked RAM
Implementation

The data width specifies the size of each data element stored in memory. This is the amount of data stored at each memory location that can be read or written in one memory access operation.

Introduction (cont'd)

- RAM capacity (C)
 - Data width (W): size of each data element stored per address

The depth of a memory refers to the number of memory locations available for storing data, effectively determining how many individual data elements the RAM can hold.

Introduction (cont'd)

- RAM capacity (C)
 - Data width (W): size of each data element stored per address
 - Depth (D): number of addressable memory locations

Usually, memory depth is defined by the width of its address bus, that is, its address width A . However, strictly speaking it is not required that a memory array really has locations for all 2^A possible address values.

Introduction (cont'd)

- RAM capacity (C)
 - Data width (W): size of each data element stored per address
 - Depth (D): number of addressable memory locations
 - usually defined by the address width A
 - $\Rightarrow D = 2^A$

Together, the product of the data width and depth define the total storage capacity of the RAM.

Introduction (cont'd)

- RAM capacity (C)
 - Data width (W): size of each data element stored per address
 - Depth (D): number of addressable memory locations
 - usually defined by the address width A
 - $\Rightarrow D = 2^A$
 - $C = W \times D$

In addition to capacity, RAM is also characterized by the types and number of independent memory access ports it supports. A single memory port supports one operation at a time, usually in a single clock cycle.

Introduction (cont'd)

- RAM capacity (C)
 - Data width (W): size of each data element stored per address
 - Depth (D): number of addressable memory locations
 - usually defined by the address width A
 - $\Rightarrow D = 2^A$
 - $C = W \times D$
- Memory access port types

These include read ports for retrieving stored data, write ports for inserting new data, and combined read/write ports, which allow both operations to be performed through a single port.

Introduction (cont'd)

- RAM capacity (C)
 - Data width (W): size of each data element stored per address
 - Depth (D): number of addressable memory locations
 - usually defined by the address width A
 - $\Rightarrow D = 2^A$
 - $C = W \times D$
- Memory access port types
 - read
 - write
 - read/write

- RAM capacity (C)
 - Data width (W): size of each data element stored per address
 - Depth (D): number of addressable memory locations
 - usually defined by the address width A
 - $2^A \leq D \leq 2^A$
 - $C = W \times D$
- Memory access port types
 - read
 - write
 - read/write
- Multiple independent ports are possible

Modern on-chip RAM architectures can support multiple independent ports that can be operated simultaneously.

Introduction (cont'd)

- RAM capacity (C)
 - Data width (W): size of each data element stored per address
 - Depth (D): number of addressable memory locations
 - usually defined by the address width A
 - $\Rightarrow D = 2^A$
 - $C = W \times D$
- Memory access port types
 - read
 - write
 - read/write
- Multiple independent ports are possible

- RAM capacity (C)
 - Data width (W): size of each data element stored per address
 - Depth (D): number of addressable memory locations
 - usually defined by the address width A
 - $2^A \leq D$
 - $C = W \times D$
- Memory access port types
 - read
 - write
 - read/write
- Multiple independent ports are possible
 - Simple dual-port RAM: one read and one write port

A common example is simple dual-port RAM, which features one read port and one write port, allowing simultaneous reading and writing operations. This type of RAM is very common in digital design, as it is necessary to implement FIFO buffers that can be read and written simultaneously.

Introduction (cont'd)

- RAM capacity (C)
 - Data width (W): size of each data element stored per address
 - Depth (D): number of addressable memory locations
 - usually defined by the address width A
 - $\Rightarrow D = 2^A$
 - $C = W \times D$
- Memory access port types
 - read
 - write
 - read/write
- Multiple independent ports are possible
 - Simple dual-port RAM: one read and one write port

- RAM capacity (C)
 - Data width (W): size of each data element stored per address
 - Depth (D): number of addressable memory locations
 - usually defined by the address width A
 - $2^A \leq D \leq 2^A$
 - $C = W \times D$
- Memory access port types
 - read
 - write
 - read/write
- Multiple independent ports are possible
 - Simple dual-port RAM: one read and one write port
 - True dual-port RAM: two read/write ports

A more advanced configuration, that is also very common, is true dual-port RAM, which provides two read/write ports. This design permits two fully independent read- or write-operations to occur simultaneously. In this lecture, we will look at examples for both of these types.

Introduction (cont'd)

- RAM capacity (C)
 - Data width (W): size of each data element stored per address
 - Depth (D): number of addressable memory locations
 - usually defined by the address width A
 - $\Rightarrow D = 2^A$
 - $C = W \times D$
- Memory access port types
 - read
 - write
 - read/write
- Multiple independent ports are possible
 - Simple dual-port RAM: one read and one write port
 - True dual-port RAM: two read/write ports

Dedicated on-chip memory blocks are a critical resource in FPGA design. They provide efficient storage and rapid access to data directly within the programmable fabric of the device.

Memory Blocks in FPGAs

- Memory blocks are an important FPGA resource

HWMoD
WS25

RAM

- Introduction
- FPGA Memory**
- Simple DP RAM
- True DP RAM
- Dual-Clocked RAM
- Implementation

- └ RAM in VHDL (for FPGAs)
 - └ Memory Blocks in FPGAs
 - └ **Memory Blocks in FPGAs**

- Memory blocks are an important FPGA resource
- Logic-based memory (often) impractical
- Highest speed/lowest latency memory in a design

Attempting to implement large memories using the storage elements provided by general-purpose logic elements in an FPGA would require a significant number of resources, which is expensive and often impractical. Logic-based memory consumes excessive chip area and power, leaving fewer resources available for other tasks, which is why FPGAs are designed with dedicated memory blocks optimized for high-density storage and efficient access.

Memory Blocks in FPGAs

- Memory blocks are an important FPGA resource
 - Logic-based memory (often) impractical
 - Highest speed/lowest latency memory in a design

HWMoD
WS25

RAM
Introduction
FPGA Memory
Simple DP RAM
True DP RAM
Dual-Clocked RAM
Implementation

- └ RAM in VHDL (for FPGAs)
 - └ Memory Blocks in FPGAs
 - └ **Memory Blocks in FPGAs**

- Memory blocks are an important FPGA resource
- Logic-based memory (often) impractical
- Highest speed/lowest latency memory in a design

Implementing memory using general-purpose logic only makes sense for memories which are significantly smaller than the available minimum memory block sizes in a given FPGA, or if a certain critical performance goal has to be met. However, this is rarely a decision that you as the developer have to make, but is rather left to the synthesis tool.

Memory Blocks in FPGAs

- Memory blocks are an important FPGA resource
 - Logic-based memory (often) impractical
 - Highest speed/lowest latency memory in a design

HWMoD
WS25

RAM

- Introduction
- FPGA Memory**
- Simple DP RAM
- True DP RAM
- Dual-Clocked RAM
- Implementation

One of the key features of memory blocks in FPGAs is their high configurability and versatility.

Memory Blocks in FPGAs

- Memory blocks are an important FPGA resource
 - Logic-based memory (often) impractical
 - Highest speed/lowest latency memory in a design
- Highly configurable in terms of

One physical memory block on the chip can be used with a wide range of different data and address widths.

Memory Blocks in FPGAs

- Memory blocks are an important FPGA resource
 - Logic-based memory (often) impractical
 - Highest speed/lowest latency memory in a design
- Highly configurable in terms of
 - data width
 - address width

HWMoD
WS25

RAM

Introduction
FPGA Memory
Simple DP RAM
True DP RAM
Dual-Clocked RAM
Implementation

Additionally, often various access port configurations are supported, allowing memory blocks to be tailored to meet specific application needs. Usually, FPGA block RAM supports at least simple, but commonly also true dual-port modes for simultaneous read and write operations. Often it is also possible to use different data and address widths on different ports of a block RAM.

Memory Blocks in FPGAs

- Memory blocks are an important FPGA resource
 - Logic-based memory (often) impractical
 - Highest speed/lowest latency memory in a design
- Highly configurable in terms of
 - data width
 - address width
 - number and type of access ports
 - control signals (e.g., read/write/byte enable)

RAM in VHDL (for FPGAs)

Memory Blocks in FPGAs

Memory Blocks in FPGAs

- Memory blocks are an important FPGA resource
 - Logic-based memory (often impractical)
 - Highest speed/lowest latency memory in a design
- Highly configurable in terms of
 - data width
 - address width
 - number and type of access ports
 - control signals (e.g., read/write/byte enable)
 - parity bits (error detection)

Some memory blocks even include built-in support for parity bits, which are essential for error detection and maintaining data integrity in critical systems.

Memory Blocks in FPGAs

- Memory blocks are an important FPGA resource
 - Logic-based memory (often) impractical
 - Highest speed/lowest latency memory in a design
- Highly configurable in terms of
 - data width
 - address width
 - number and type of access ports
 - control signals (e.g., read/write/byte enable)
 - parity bits (error detection)

HWMoD
WS25

RAM

Introduction
FPGA Memory
Simple DP RAM
True DP RAM
Dual-Clocked RAM
Implementation

RAM in VHDL (for FPGAs)

Memory Blocks in FPGAs

Memory Blocks in FPGAs

- Memory blocks are an important FPGA resource
 - Logic-based memory (often) impractical
 - Highest speed/lowest latency memory in a design
- Highly configurable in terms of
 - data width
 - address width
 - number and type of access ports
 - control signals (e.g., read/write/byte enable)
 - parity bits (error detection)
- Memory in modern FPGAs is (almost) always synchronous

Another defining characteristic of memory blocks in modern FPGAs is their synchronous operation.

Memory Blocks in FPGAs

- Memory blocks are an important FPGA resource
 - Logic-based memory (often) impractical
 - Highest speed/lowest latency memory in a design
- Highly configurable in terms of
 - data width
 - address width
 - number and type of access ports
 - control signals (e.g., read/write/byte enable)
 - parity bits (error detection)
- Memory in modern FPGAs is (almost) always synchronous

HWMoD
WS25

RAM

Introduction
FPGA Memory
Simple DP RAM
True DP RAM
Dual-Clocked RAM
Implementation

RAM in VHDL (for FPGAs)

Memory Blocks in FPGAs

Memory Blocks in FPGAs

- Memory blocks are an important FPGA resource
 - Logic-based memory (often) impractical
 - Highest speed/lowest latency memory in a design
- Highly configurable in terms of
 - data width
 - address width
 - number and type of access ports
 - control signals (e.g., read/write/byte enable)
 - parity bits (error detection)
- Memory in modern FPGAs is (almost) always synchronous
 - Read and write operations only happen at a clock edge

In synchronous memory, read and write actions occur only at the active clock edge, allowing for a seamless integration with other synchronous components and simplifying timing analysis.

Memory Blocks in FPGAs

- Memory blocks are an important FPGA resource
 - Logic-based memory (often) impractical
 - Highest speed/lowest latency memory in a design
- Highly configurable in terms of
 - data width
 - address width
 - number and type of access ports
 - control signals (e.g., read/write/byte enable)
 - parity bits (error detection)
- Memory in modern FPGAs is (almost) always synchronous
 - Read and write operations only happen at a clock edge

HWMoD
WS25

RAM

Introduction
FPGA Memory
Simple DP RAM
True DP RAM
Dual-Clocked RAM
Implementation

RAM in VHDL (for FPGAs)

Memory Blocks in FPGAs

Memory Blocks in FPGAs

- Memory blocks are an important FPGA resource
 - Logic-based memory (often) impractical
 - Highest speed/lowest latency memory in a design
- Highly configurable in terms of
 - data width
 - address width
 - number and type of access ports
 - control signals (e.g., read/write/byte enable)
 - parity bits (error detection)
- Memory in modern FPGAs is (almost) always synchronous
 - Read and write operations only happen at a clock edge
 - Some older FPGAs support asynchronous memory

In contrast, older FPGA architectures sometimes included asynchronous memory, which allowed operations to occur independently of the clock signal. While asynchronous memory provided more flexibility in certain contexts, it is less compatible with modern high-speed digital designs, where synchronization and timing consistency are paramount.

Memory Blocks in FPGAs

- Memory blocks are an important FPGA resource
 - Logic-based memory (often) impractical
 - Highest speed/lowest latency memory in a design
- Highly configurable in terms of
 - data width
 - address width
 - number and type of access ports
 - control signals (e.g., read/write/byte enable)
 - parity bits (error detection)
- Memory in modern FPGAs is (almost) always synchronous
 - Read and write operations only happen at a clock edge
 - Some older FPGAs support asynchronous memory

HWMoD
WS25

RAM

Introduction
FPGA Memory
Simple DP RAM
True DP RAM
Dual-Clocked RAM
Implementation

- └ RAM in VHDL (for FPGAs)
- └ Memory Blocks in FPGAs
- └ Intel FPGAs

Table 3. Embedded Memory Blocks in Intel FPGA Devices

Device Family	MLAB (640 bits)	Memory Block Type				Logic Cell (LC)
		M9K (9 Kbits)	M144K (144 Kbits)	M10K (10 Kbits)	M20K (20 Kbits)	
Arria® II GX	Yes	Yes	-	-	-	Yes
Arria II GZ	Yes	Yes	Yes	-	-	Yes
Arria V	Yes	-	-	Yes	-	Yes
Intel Arria 10	Yes	-	-	-	Yes	Yes
Cyclone® IV	-	Yes	-	-	-	Yes
Cyclone V	Yes	-	-	Yes	-	Yes
Intel Cyclone 10 LP	-	Yes	-	-	-	Yes
Intel Cyclone 10 GX	Yes	-	-	-	Yes	Yes
MAX® II	-	-	-	-	-	Yes
Intel MAX 10	-	Yes	-	-	-	Yes
Stratix IV	Yes	Yes	Yes	-	-	Yes
Stratix V	Yes	-	-	-	Yes	Yes

Source: Embedded Memory User Guide

This slide shows an overview of the available memory resources in the various Intel FPGA device families. It outlines the types of memory blocks and their availability across device families.

Intel FPGAs

Table 3. Embedded Memory Blocks in Intel FPGA Devices

Device Family	Memory Block Type					
	MLAB (640 bits)	M9K (9 Kbits)	M144K (144 Kbits)	M10K (10 Kbits)	M20K (20 Kbits)	Logic Cell (LC)
Arria® II GX	Yes	Yes	-	-	-	Yes
Arria II GZ	Yes	Yes	Yes	-	-	Yes
Arria V	Yes	-	-	Yes	-	Yes
Intel Arria 10	Yes	-	-	-	Yes	Yes
Cyclone® IV	-	Yes	-	-	-	Yes
Cyclone V	Yes	-	-	Yes	-	Yes
Intel Cyclone 10 LP	-	Yes	-	-	-	Yes
Intel Cyclone 10 GX	Yes	-	-	-	Yes	Yes
MAX® II	-	-	-	-	-	Yes
Intel MAX 10	-	Yes	-	-	-	Yes
Stratix IV	Yes	Yes	Yes	-	-	Yes
Stratix V	Yes	-	-	-	Yes	Yes

Source: Embedded Memory User Guide

HWMoD
WS25

RAM
Introduction
FPGA Memory
Simple DP RAM
True DP RAM
Dual-Clocked RAM
Implementation

- └ RAM in VHDL (for FPGAs)
- └ Memory Blocks in FPGAs
- └ Intel FPGAs

Table 3. Embedded Memory Blocks in Intel FPGA Devices

Device Family	MLAB (640 bits)	M9K (9 Kbits)	M144K (144 Kbits)	M10K (10 Kbits)	M20K (20 Kbits)	Logic Cell (LC)
Arria® II GX	Yes	Yes	-	-	-	Yes
Arria II GZ	Yes	Yes	Yes	-	-	Yes
Arria V	Yes	-	-	Yes	-	Yes
Intel Arria 10	Yes	-	-	-	Yes	Yes
Cyclone® IV	-	Yes	-	-	-	Yes
Cyclone V	Yes	-	-	Yes	-	Yes
Intel Cyclone 10 LP	-	Yes	-	-	-	Yes
Intel Cyclone 10 GX	Yes	-	-	-	Yes	Yes
MAX® II	-	-	-	-	-	Yes
Intel MAX 10	-	Yes	-	-	-	Yes
Stratix IV	Yes	Yes	Yes	-	-	Yes
Stratix V	Yes	-	-	-	Yes	Yes

Source: Embedded Memory User Guide

For instance, the Cyclone IV, which we use in the exercise part of this course, supports logic-based memory as well as dedicated M9K memory blocks.

Intel FPGAs

Table 3. Embedded Memory Blocks in Intel FPGA Devices

Device Family	Memory Block Type					
	MLAB (640 bits)	M9K (9 Kbits)	M144K (144 Kbits)	M10K (10 Kbits)	M20K (20 Kbits)	Logic Cell (LC)
Arria® II GX	Yes	Yes	-	-	-	Yes
Arria II GZ	Yes	Yes	Yes	-	-	Yes
Arria V	Yes	-	-	Yes	-	Yes
Intel Arria 10	Yes	-	-	-	Yes	Yes
Cyclone® IV	-	Yes	-	-	-	Yes
Cyclone V	Yes	-	-	Yes	-	Yes
Intel Cyclone 10 LP	-	Yes	-	-	-	Yes
Intel Cyclone 10 GX	Yes	-	-	-	Yes	Yes
MAX® II	-	-	-	-	-	Yes
Intel MAX 10	-	Yes	-	-	-	Yes
Stratix IV	Yes	Yes	Yes	-	-	Yes
Stratix V	Yes	-	-	-	Yes	Yes

Source: Embedded Memory User Guide

HWMoD
WS25

RAM
Introduction
FPGA Memory
Simple DP RAM
True DP RAM
Dual-Clocked RAM
Implementation

- └ RAM in VHDL (for FPGAs)
- └ Memory Blocks in FPGAs
- └ Intel FPGAs

Table 3. Embedded Memory Blocks in Intel FPGA Devices

Device Family	MLAB (640 bits)	M9K (9 Kbits)	M144K (144 Kbits)	M10K (10 Kbits)	M20K (20 Kbits)	Logic Cell (LC)
Arria® II GX	Yes	Yes	-	-	-	Yes
Arria II GZ	Yes	Yes	Yes	-	-	Yes
Arria V	Yes	-	-	Yes	-	Yes
Intel Arria 10	Yes	-	-	-	Yes	Yes
Cyclone® IV	-	Yes	-	-	-	Yes
Cyclone V	Yes	-	-	Yes	-	Yes
Intel Cyclone 10 LP	-	Yes	-	-	-	Yes
Intel Cyclone 10 GX	Yes	-	-	-	Yes	Yes
MAX® II	-	-	-	-	-	Yes
Intel MAX 10	-	Yes	-	-	-	Yes
Stratix IV	Yes	Yes	Yes	-	-	Yes
Stratix V	Yes	-	-	-	Yes	Yes

Source: Embedded Memory User Guide

Other, more recent devices, such as the Arria 10 utilize larger M20K blocks for enhanced memory capacity. The table shows that memory resources in FPGA are quite diverse and vary greatly between device families.

Intel FPGAs

Table 3. Embedded Memory Blocks in Intel FPGA Devices

Device Family	Memory Block Type					
	MLAB (640 bits)	M9K (9 Kbits)	M144K (144 Kbits)	M10K (10 Kbits)	M20K (20 Kbits)	Logic Cell (LC)
Arria® II GX	Yes	Yes	-	-	-	Yes
Arria II GZ	Yes	Yes	Yes	-	-	Yes
Arria V	Yes	-	-	Yes	-	Yes
Intel Arria 10	Yes	-	-	-	Yes	Yes
Cyclone® IV	-	Yes	-	-	-	Yes
Cyclone V	Yes	-	-	Yes	-	Yes
Intel Cyclone 10 LP	-	Yes	-	-	-	Yes
Intel Cyclone 10 GX	Yes	-	-	-	Yes	Yes
MAX® II	-	-	-	-	-	Yes
Intel MAX 10	-	Yes	-	-	-	Yes
Stratix IV	Yes	Yes	Yes	-	-	Yes
Stratix V	Yes	-	-	-	Yes	Yes

Source: Embedded Memory User Guide

HWMoD
WS25

RAM
Introduction
FPGA Memory
Simple DP RAM
True DP RAM
Dual-Clocked RAM
Implementation

RAM in VHDL (for FPGAs)

Simple Dual-Port RAM

Simple Dual-Port RAM

```
1 entity simple_dp_ram is
2   generic (
3     ADDR_WIDTH : positive;
4     DATA_WIDTH : positive;
5     WR_EN :
6       type t is std_ulogic;
7       type t is std_ulogic;
8     RD_EN : std_ulogic;
9     WR_ADDR : in std_ulogic_vector(ADDR_WIDTH - 1 downto 0);
10    RD_ADDR : in std_ulogic_vector(ADDR_WIDTH - 1 downto 0);
11    WR_DATA : out std_ulogic_vector(DATA_WIDTH - 1 downto 0);
12    RD_DATA : out std_ulogic_vector(DATA_WIDTH - 1 downto 0);
13  );
14  port (
15    clk : in std_ulogic;
16    wr_en : in std_ulogic;
17    rd_en : in std_ulogic;
18    wr_addr : in std_ulogic_vector(ADDR_WIDTH - 1 downto 0);
19    rd_addr : in std_ulogic_vector(ADDR_WIDTH - 1 downto 0);
20    wr_data : out std_ulogic_vector(DATA_WIDTH - 1 downto 0);
21    rd_data : out std_ulogic_vector(DATA_WIDTH - 1 downto 0);
22  );
23 end entity;
```

Let us now look at some VHDL code. This slide shows how an entity declaration for a typical simple dual-port memory in VHDL can look like. Of course the naming convention for the signal names is not standardized, and you will find many variations in practice. In this lecture we always use a common identifier to prefix the signals that belong to a specific memory port.

Simple Dual-Port RAM

```
1 entity simple_dp_ram is
2   generic (
3     ADDR_WIDTH : positive;
4     DATA_WIDTH : positive;
5   );
6   port (
7     clk : in std_ulogic;
8     -- read port
9     rd_en : in std_ulogic;
10    rd_addr : in std_ulogic_vector(ADDR_WIDTH - 1 downto 0);
11    rd_data : out std_ulogic_vector(DATA_WIDTH - 1 downto 0);
12    -- write port
13    wr_en : in std_ulogic;
14    wr_addr : in std_ulogic_vector(ADDR_WIDTH - 1 downto 0);
15    wr_data : in std_ulogic_vector(DATA_WIDTH - 1 downto 0)
16  );
17 end entity;
```

HWMoD
WS25

RAM

Introduction
FPGA Memory
Simple DP RAM
Read Access
Write Access
True DP RAM
Dual-Clocked RAM
Implementation

RAM in VHDL (for FPGAs)

Simple Dual-Port RAM

Simple Dual-Port RAM

```
1 entity simple_dp_ram is
2   generic (
3     ADDR_WIDTH : positive;
4     DATA_WIDTH : positive;
5   );
6   port (
7     clk : in std_ulogic;
8     rd_en : in std_ulogic;
9     rd_addr : in std_ulogic_vector(ADDR_WIDTH - 1 downto 0);
10    rd_data : out std_ulogic_vector(DATA_WIDTH - 1 downto 0);
11    wr_en : in std_ulogic;
12    wr_addr : in std_ulogic_vector(ADDR_WIDTH - 1 downto 0);
13    wr_data : in std_ulogic_vector(DATA_WIDTH - 1 downto 0);
14  );
15 end entity;
```

The clock signal that controls all operations on both the read and the write port.

As already explained, memory blocks in modern FPGAs are always synchronous. Hence, we need a clock input to which all memory operations are synchronized to.

Simple Dual-Port RAM

```
1 entity simple_dp_ram is
2   generic (
3     ADDR_WIDTH : positive;
4     DATA_WIDTH : positive;
5   );
6   port (
7     clk : in std_ulogic;
8     -- read port
9     rd_en : in std_ulogic;
10    rd_addr : in std_ulogic_vector(ADDR_WIDTH - 1 downto 0);
11    rd_data : out std_ulogic_vector(DATA_WIDTH - 1 downto 0);
12    -- write port
13    wr_en : in std_ulogic;
14    wr_addr : in std_ulogic_vector(ADDR_WIDTH - 1 downto 0);
15    wr_data : in std_ulogic_vector(DATA_WIDTH - 1 downto 0);
16  );
17 end entity;
```

The clock signal that controls all operations on both the read and the write port.

HWMoD
WS25

RAM

- Introduction
- FPGA Memory
- Simple DP RAM
- Read Access
- Write Access
- True DP RAM
- Dual-Clocked RAM
- Implementation

RAM in VHDL (for FPGAs)

Simple Dual-Port RAM

Simple Dual-Port RAM

```
1 entity simple_dp_ram is
2   generic (
3     ADDR_WIDTH : positive;
4     DATA_WIDTH : positive;
5     )
6   port (
7     clk : in std_ulogic;
8     rd_en : in std_ulogic;
9     rd_addr : in std_ulogic_vector(ADDR_WIDTH - 1 downto 0);
10    rd_data : out std_ulogic_vector(DATA_WIDTH - 1 downto 0);
11    wr_en : in std_ulogic;
12    wr_addr : in std_ulogic_vector(ADDR_WIDTH - 1 downto 0);
13    wr_data : in std_ulogic_vector(DATA_WIDTH - 1 downto 0);
14    );
15 end entity;
```


Memory read port

This group of signals represents the read-port of the RAM. It consists of an input for the address and an output for the read data. The read enable input (`rd_en`) is used to trigger the actual read operation. This is a signal that is not always present on RAM modules, since in some applications read should simply happen on every clock cycle.

Simple Dual-Port RAM

```
1 entity simple_dp_ram is
2   generic (
3     ADDR_WIDTH : positive;
4     DATA_WIDTH : positive;
5   );
6   port (
7     clk : in std_ulogic;
8     -- read port
9     rd_en : in std_ulogic;
10    rd_addr : in std_ulogic_vector(ADDR_WIDTH - 1 downto 0);
11    rd_data : out std_ulogic_vector(DATA_WIDTH - 1 downto 0);
12    -- write port
13    wr_en : in std_ulogic;
14    wr_addr : in std_ulogic_vector(ADDR_WIDTH - 1 downto 0);
15    wr_data : in std_ulogic_vector(DATA_WIDTH - 1 downto 0);
16  );
17 end entity;
```

Memory read port.

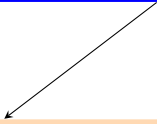

HWMoD
WS25

RAM

- Introduction
- FPGA Memory
- Simple DP RAM
- Read Access
- Write Access
- True DP RAM
- Dual-Clocked RAM
- Implementation

RAM in VHDL (for FPGAs)

Simple Dual-Port RAM

Simple Dual-Port RAM

```
1 entity simple_dp_ram is
2 generic (
3   ADDR_WIDTH : positive;
4   DATA_WIDTH : positive;
5 )
6 port (
7   clk : in std_ulogic;
8   rd_en : in std_ulogic;
9   rd_addr : in std_ulogic_vector(ADDR_WIDTH - 1 downto 0);
10  rd_data : out std_ulogic_vector(DATA_WIDTH - 1 downto 0);
11  wr_en : in std_ulogic;
12  wr_addr : in std_ulogic_vector(ADDR_WIDTH - 1 downto 0);
13  wr_data : in std_ulogic_vector(DATA_WIDTH - 1 downto 0);
14 );
15 end entity;
```

Memory write port

The last group of signals represents the write-port. Here, both the data and address signals are inputs. The write-enable (`wr_en`) signal controls when data is actually written to memory. Sometimes RAM also features byte-enable signals on the write-port to only selectively write certain parts of the input data.

Simple Dual-Port RAM

HWMoD
WS25

RAM

- Introduction
- FPGA Memory
- Simple DP RAM
- Read Access
- Write Access
- True DP RAM
- Dual-Clocked RAM
- Implementation

```
1 entity simple_dp_ram is
2 generic (
3   ADDR_WIDTH : positive;
4   DATA_WIDTH : positive;
5 );
6 port (
7   clk : in std_ulogic;
8   -- read port
9   rd_en : in std_ulogic;
10  rd_addr : in std_ulogic_vector(ADDR_WIDTH - 1 downto 0);
11  rd_data : out std_ulogic_vector(DATA_WIDTH - 1 downto 0);
12  -- write port
13  wr_en : in std_ulogic;
14  wr_addr : in std_ulogic_vector(ADDR_WIDTH - 1 downto 0);
15  wr_data : in std_ulogic_vector(DATA_WIDTH - 1 downto 0);
16 );
17 end entity;
```

Memory write port.

- RAM in VHDL (for FPGAs)
 - Simple Dual-Port RAM
 - Read Access**

```
clk  —
rd_en —
rd_addr [D/C]
rd_data [D/C]
```

Now that we know the interface signals, we can discuss how to interface with the shown RAM entity. For that purpose we assume that the RAM has a latency of one clock cycle. This means that the respective data is available in the next clock cycle from the point in time when the read was issued. Initially, both the input address as well as the output data are in a "don't care" state, which just means that their actual values are irrelevant for the purpose of this example. The read enable signal is zero.

Read Access

HWMoD
WS25

RAM

- Introduction
- FPGA Memory
- Simple DP RAM
- Read Access**
- Write Access
- True DP RAM
- Dual-Clocked RAM
- Implementation

```
clk  —
rd_en —
rd_addr [D/C]
rd_data [D/C]
```

- RAM in VHDL (for FPGAs)
 - Simple Dual-Port RAM
 - Read Access**




Now, let's say we want to read the data stored in the memory at address a_0 . Hence, we apply the respective address to the address input of the read port and set the read enable signal to high.

Read Access


HWMoD
WS25

RAM

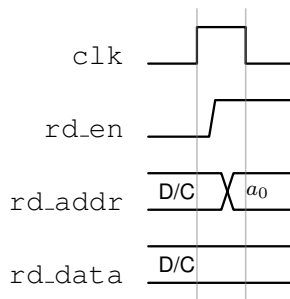- Introduction
- FPGA Memory
- Simple DP RAM
- Read Access**
- Write Access
- True DP RAM
- Dual-Clocked RAM
- Implementation



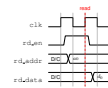- └ RAM in VHDL (for FPGAs)
 - └ Simple Dual-Port RAM
 - └ **Read Access**




At the next rising clock edge – marked in red in the timing diagram – the RAM can now sample these inputs and output the value stored at address a_0 .

Read Access


HWMoD
WS25

RAM

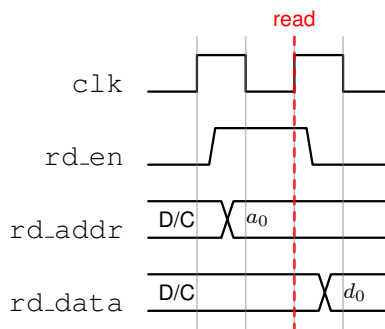- Introduction
- FPGA Memory
- Simple DP RAM
- Read Access**
- Write Access
- True DP RAM
- Dual-Clocked RAM
- Implementation



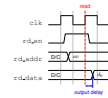
- └ RAM in VHDL (for FPGAs)
 - └ Simple Dual-Port RAM
 - └ **Read Access**



Note that, as also indicated in the timing diagram, this does not happen instantaneously but rather takes some time due to the intrinsic propagation delays and setup times associated with the memory access. The timing analysis has to take this access time value into account. However, we can safely assume that the value is available at the next rising clock edge. In this clock cycle no new read operation is performed on the memory, hence the read enable signal is reset to low.

Read Access

HWMoD
WS25

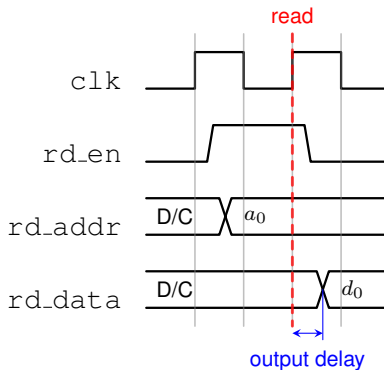

RAM

- Introduction
- FPGA Memory
- Simple DP RAM
- Read Access**
- Write Access
- True DP RAM
- Dual-Clocked RAM
- Implementation

- └ RAM in VHDL (for FPGAs)
 - └ Simple Dual-Port RAM
 - └ **Read Access**




Now a second read is performed – this time on address a_1 . Note that since this read will only be initiated at the next rising clock edge the memory still outputs the value of the previous read operation.

Read Access


HWMoD
WS25

RAM

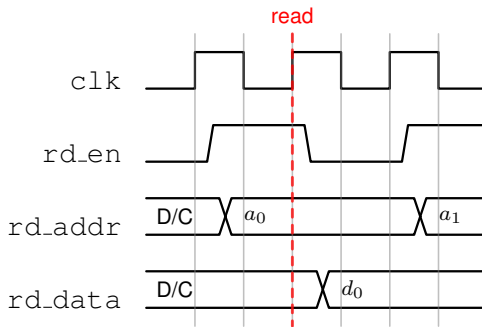- Introduction
- FPGA Memory
- Simple DP RAM
- Read Access**
- Write Access
- True DP RAM
- Dual-Clocked RAM
- Implementation



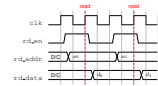- └ RAM in VHDL (for FPGAs)
 - └ Simple Dual-Port RAM
 - └ **Read Access**




Again the read value can be retrieved after the next rising clock edge.

Read Access


HWMoD
WS25

RAM

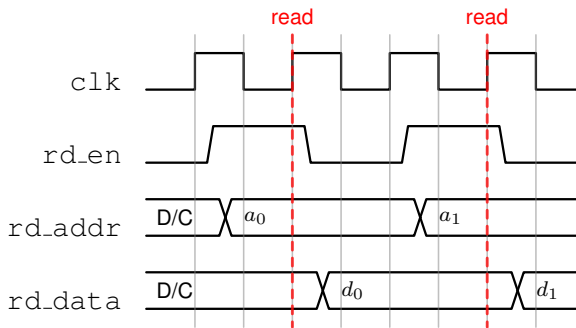- Introduction
- FPGA Memory
- Simple DP RAM
- Read Access**
- Write Access
- True DP RAM
- Dual-Clocked RAM
- Implementation




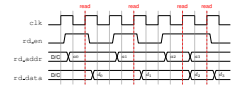- └ RAM in VHDL (for FPGAs)
 - └ Simple Dual-Port RAM
 - └ **Read Access**



Reads can also be performed back-to-back, that is in consecutive clock cycles. This is shown for the read of addresses a_2 and a_3 in the timing diagram.

Read Access

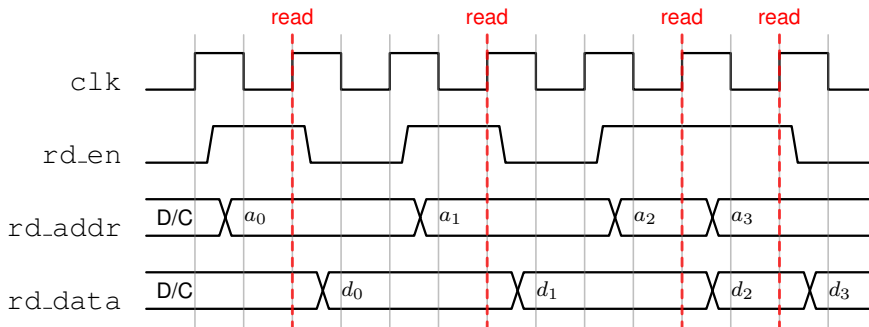


HWMoD
WS25

RAM

- Introduction
- FPGA Memory
- Simple DP RAM
- Read Access**
- Write Access
- True DP RAM
- Dual-Clocked RAM
- Implementation

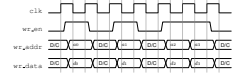- RAM in VHDL (for FPGAs)
 - Simple Dual-Port RAM
 - Write Access**




Now, let's turn to the write access, which is a little simpler than the read access.

Write Access


HWMoD
WS25

RAM

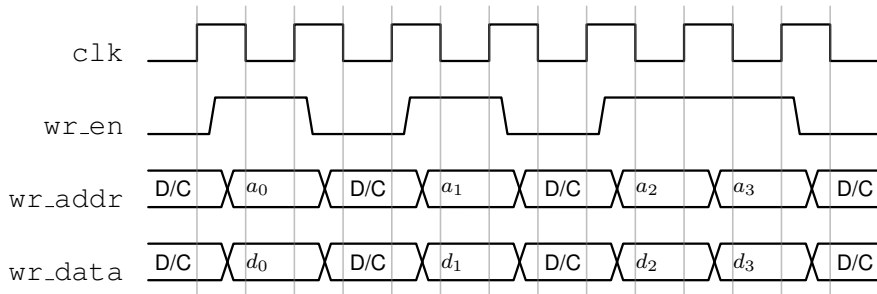- Introduction
- FPGA Memory
- Simple DP RAM
- Read Access
- Write Access**
- True DP RAM
- Dual-Clocked RAM
- Implementation



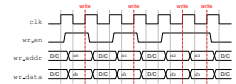- RAM in VHDL (for FPGAs)
 - Simple Dual-Port RAM
 - Write Access**




Whenever data should be written, the address and the associated data have to be applied at the respective inputs of the memory. If the write-enable signal (wr_en) is high at the rising edge of the clock signal, the data and address signals are sampled leading to the data being written to memory.

Write Access


HWMoD
WS25

RAM

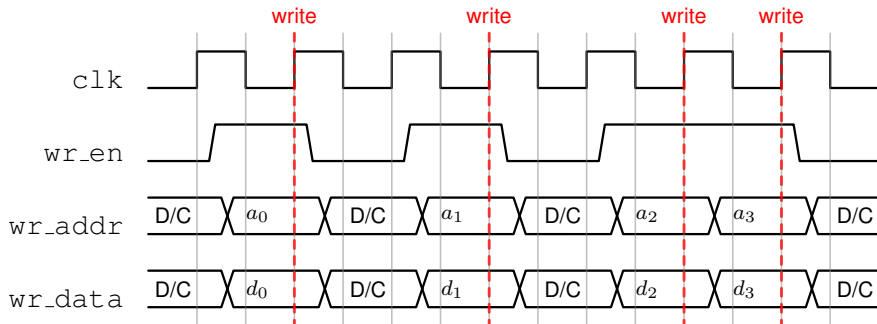- Introduction
- FPGA Memory
- Simple DP RAM
- Read Access
- Write Access**
- True DP RAM
- Dual-Clocked RAM
- Implementation



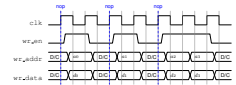- RAM in VHDL (for FPGAs)
 - Simple Dual-Port RAM
 - Write Access**




In all other cases the memory simply ignores the values of the data and address signals, which is indicated by the "don't care" values in the timing diagram. Please pause the video at this point and make sure that you understand the shown timing diagram.

Write Access

HWMoD
WS25

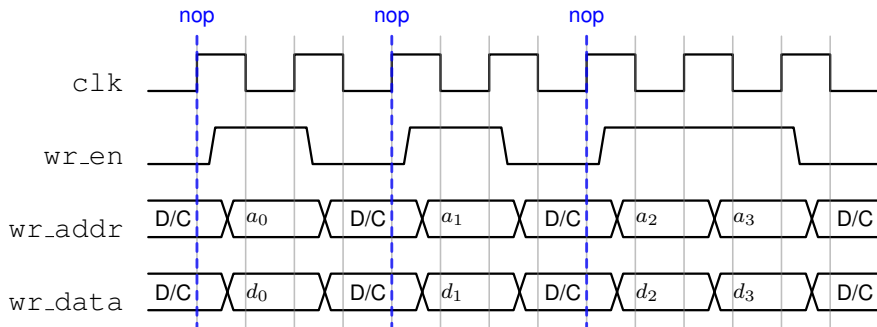RAM
Introduction
FPGA Memory
Simple DP RAM
Read Access
Write Access
True DP RAM
Dual-Clocked RAM
Implementation



RAM in VHDL (for FPGAs)

True Dual-Port RAM

True Dual-Port RAM

```

1 entity true_dp_ram is
2   generic (
3     ADDR_WIDTH : positive;
4     DATA_WIDTH : positive;
5     M0 :
6     port (
7       clk : in std_ulogic;
8       rd0_en : in std_ulogic;
9       wr0_en : in std_ulogic;
10      rd0_addr : in std_ulogic_vector(ADDR_WIDTH - 1 downto 0);
11      wr0_data : out std_ulogic_vector(DATA_WIDTH - 1 downto 0);
12      rd0_data : out std_ulogic_vector(DATA_WIDTH - 1 downto 0);
13      rd1_en : in std_ulogic;
14      wr1_en : in std_ulogic;
15      rd1_addr : in std_ulogic_vector(ADDR_WIDTH - 1 downto 0);
16      wr1_data : out std_ulogic_vector(DATA_WIDTH - 1 downto 0);
17      rd1_data : out std_ulogic_vector(DATA_WIDTH - 1 downto 0);
18    );
19 end entity;

```

This slide shows an example for the interface of a true dual-port RAM.

True Dual-Port RAM

```

1 entity true_dp_ram is
2   generic (
3     ADDR_WIDTH : positive;
4     DATA_WIDTH : positive;
5   );
6   port (
7     clk : in std_ulogic;
8     -- read/write port 0
9     rw0_rd_en : in std_ulogic;
10    rw0_wr_en : in std_ulogic;
11    rw0_addr : in std_ulogic_vector(ADDR_WIDTH - 1 downto 0);
12    rw0_wr_data : out std_ulogic_vector(DATA_WIDTH - 1 downto 0);
13    rw0_rd_data : out std_ulogic_vector(DATA_WIDTH - 1 downto 0);
14    -- read/write port 1
15    rw1_rd_en : in std_ulogic;
16    rw1_wr_en : in std_ulogic;
17    rw1_addr : in std_ulogic_vector(ADDR_WIDTH - 1 downto 0);
18    rw1_wr_data : out std_ulogic_vector(DATA_WIDTH - 1 downto 0);
19    rw1_rd_data : out std_ulogic_vector(DATA_WIDTH - 1 downto 0);
20  );
21 end entity;

```

HWMoD
WS25

RAM

Introduction
FPGA Memory
Simple DP RAM
True DP RAM
Dual-Clocked RAM
Implementation

RAM in VHDL (for FPGAs)

- True Dual-Port RAM
- True Dual-Port RAM

```
1 entity True_DP_RAM is
2   generic (
3     ADDR_WIDTH : positive;
4     DATA_WIDTH : positive
5   );
6   port (
7     clk : in std_ulogic;
8     -- read/write port 0
9     rw0_rd_en : in std_ulogic;
10    rw0_wr_en : in std_ulogic;
11    rw0_addr : in std_ulogic_vector(ADDR_WIDTH - 1 downto 0);
12    rw0_wr_data : out std_ulogic_vector(DATA_WIDTH - 1 downto 0);
13    rw0_rd_data : out std_ulogic_vector(DATA_WIDTH - 1 downto 0);
14    -- read/write port 1
15    rw1_rd_en : in std_ulogic;
16    rw1_wr_en : in std_ulogic;
17    rw1_addr : in std_ulogic_vector(ADDR_WIDTH - 1 downto 0);
18    rw1_wr_data : out std_ulogic_vector(DATA_WIDTH - 1 downto 0);
19    rw1_rd_data : out std_ulogic_vector(DATA_WIDTH - 1 downto 0)
20  );
21 end entity;
```

True read/write memory port

Notice that in our example both ports consist of the exact same signals. As already mentioned, this is not a strict requirement, as it is also possible and supported by many FPGAs to use different interface configurations on both ports.


True Dual-Port RAM

HWMMod
WS25

- RAM
- Introduction
- FPGA Memory
- Simple DP RAM
- True DP RAM
- Dual-Clocked RAM
- Implementation

```
1 entity true_dp_ram is
2   generic (
3     ADDR_WIDTH : positive;
4     DATA_WIDTH : positive
5   );
6   port (
7     clk : in std_ulogic;
8     -- read/write port 0
9     rw0_rd_en : in std_ulogic;
10    rw0_wr_en : in std_ulogic;
11    rw0_addr : in std_ulogic_vector(ADDR_WIDTH - 1 downto 0);
12    rw0_wr_data : out std_ulogic_vector(DATA_WIDTH - 1 downto 0);
13    rw0_rd_data : out std_ulogic_vector(DATA_WIDTH - 1 downto 0);
14    -- read/write port 1
15    rw1_rd_en : in std_ulogic;
16    rw1_wr_en : in std_ulogic;
17    rw1_addr : in std_ulogic_vector(ADDR_WIDTH - 1 downto 0);
18    rw1_wr_data : out std_ulogic_vector(DATA_WIDTH - 1 downto 0);
19    rw1_rd_data : out std_ulogic_vector(DATA_WIDTH - 1 downto 0)
20  );
21 end entity;
```

First read/write memory port.

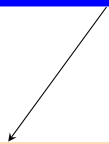

RAM in VHDL (for FPGAs)

- True Dual-Port RAM
- True Dual-Port RAM

```
1 entity True_DP_RAM is
2   generic (
3     ADDR_WIDTH : positive;
4     DATA_WIDTH : positive;
5     M0 :
6     M1 :
7     M2 :
8     M3 :
9     M4 :
10    M5 :
11    M6 :
12    M7 :
99    M94 :
100   M95 :
101   M96 :
102   M97 :
999   M994 :
1000  M995 :
1001  M996 :
1002  M997 :
1209  M1204 :
12
```

In practice, it is sometimes required to access one RAM block from two different clock domains of a design. Such scenarios often arise in clock-domain-crossing interfaces, which are crucial in complex systems where different subsystems operate on distinct clock frequencies. These situations require, what is referred to as dual-clock RAM.

Dual-Clock RAM

HWMoD
WS25

RAM

Introduction
FPGA Memory
Simple DP RAM
True DP RAM
Dual-Clocked RAM
Implementation

- Separate/independent clock for each port of a dual-port memory ⇒ dual-clock memory
- Use case: clock-domain-crossing interfaces

Most modern FPGA block RAMs provide built-in support for such dual-clock operations, making them well-suited for such scenarios.

Dual-Clock RAM

HWMoD
WS25

RAM

Introduction
FPGA Memory
Simple DP RAM
True DP RAM
Dual-Clocked RAM
Implementation

- Separate/independent clock for each port of a dual-port memory ⇒ dual-clock memory
- Use case: clock-domain-crossing interfaces
- Usually supported by FPGA block RAM

However, a key consideration when using dual-clock memory is the potential issue of simultaneous read and write operations targeting the same memory location. Such conflicts must be handled carefully to avoid undefined or erroneous behavior. Implementing robust synchronization and arbitration mechanisms is crucial to ensure reliable operation in these scenarios.

Dual-Clock RAM

HWMoD
WS25

RAM

Introduction
FPGA Memory
Simple DP RAM
True DP RAM
Dual-Clocked RAM
Implementation

- Separate/independent clock for each port of a dual-port memory ⇒ dual-clock memory
- Use case: clock-domain-crossing interfaces
- Usually supported by FPGA block RAM
- Simultaneous read and write to the same location must be handled carefully

Hence, dual-clock memory is often used in the form of dual-clock or bisynchronous FIFOs. Bisynchronous FIFOs are an important tool in a designer's toolbox and heavily used for clock-domain-crossing interfaces.

Dual-Clock RAM

HWMoD
WS25

RAM

Introduction
FPGA Memory
Simple DP RAM
True DP RAM
Dual-Clocked RAM
Implementation

- Separate/independent clock for each port of a dual-port memory ⇒ dual-clock memory
- Use case: clock-domain-crossing interfaces
- Usually supported by FPGA block RAM
- Simultaneous read and write to the same location must be handled carefully
- ⇒ dual-clocked/bisynchronous FIFOs

RAM in VHDL (for FPGAs)

Dual-Clock RAM

Dual-Clocked RAM - Example

```
1 entity dualclock_dp_ram is
2
3   generic (
4     ADDR_WIDTH : positive;
5     DATA_WIDTH : positive;
6   );
7
8   port (
9     -- read port
10    rd_clk : in std_ulogic;
11    rd_en  : in std_ulogic;
12    rd_addr : in std_ulogic_vector(ADDR_WIDTH - 1 downto 0);
13    rd_data : out std_ulogic_vector(DATA_WIDTH - 1 downto 0);
14
15    -- write port
16    wr_clk : in std_ulogic;
17    wr_en  : in std_ulogic;
18    wr_addr : in std_ulogic_vector(ADDR_WIDTH - 1 downto 0);
19    wr_data : in std_ulogic_vector(DATA_WIDTH - 1 downto 0);
20  );
21 end entity;
```

This slide shows how a dual-clock version of the simple dual-port RAM from before can look like.

Dual-Clocked RAM - Example

```
1 entity dualclock_dp_ram is
2   generic (
3     ADDR_WIDTH : positive;
4     DATA_WIDTH : positive
5   );
6   port (
7     -- read port
8     rd_clk : in std_ulogic;
9     rd_en  : in std_ulogic;
10    rd_addr : in std_ulogic_vector(ADDR_WIDTH - 1 downto 0);
11    rd_data : out std_ulogic_vector(DATA_WIDTH - 1 downto 0);
12    -- write port
13    wr_clk : in std_ulogic;
14    wr_en  : in std_ulogic;
15    wr_addr : in std_ulogic_vector(ADDR_WIDTH - 1 downto 0);
16    wr_data : in std_ulogic_vector(DATA_WIDTH - 1 downto 0)
17  );
18 end entity;
```

HWMoD
WS25

RAM

Introduction
FPGA Memory
Simple DP RAM
True DP RAM
Dual-Clocked RAM
Implementation

RAM in VHDL (for FPGAs)

Dual-Clock RAM

Dual-Clocked RAM - Example

```
1 entity dualclock_dp_ram is
2
3   generic
4     ADDR_WIDTH : positive;
5     DATA_WIDTH : positive;
6   );
7   port
8     rd_clk : in std_ulogic;
9     rd_en : in std_ulogic;
10    rd_addr : in std_ulogic_vector(ADDR_WIDTH - 1 downto 0);
11    rd_data : out std_ulogic_vector(DATA_WIDTH - 1 downto 0);
12    -- write port
13    wr_clk : in std_ulogic;
14    wr_en : in std_ulogic;
15    wr_addr : in std_ulogic_vector(ADDR_WIDTH - 1 downto 0);
16    wr_data : in std_ulogic_vector(DATA_WIDTH - 1 downto 0);
17  );
18 end entity;
```

Notice that instead of one clock input, now both the read and the write port have their own separate clock signals.

Dual-Clocked RAM - Example

```
1 entity dualclock_dp_ram is
2   generic (
3     ADDR_WIDTH : positive;
4     DATA_WIDTH : positive
5   );
6   port (
7     -- read port
8     rd_clk : in std_ulogic;
9     rd_en : in std_ulogic;
10    rd_addr : in std_ulogic_vector(ADDR_WIDTH - 1 downto 0);
11    rd_data : out std_ulogic_vector(DATA_WIDTH - 1 downto 0);
12    -- write port
13    wr_clk : in std_ulogic;
14    wr_en : in std_ulogic;
15    wr_addr : in std_ulogic_vector(ADDR_WIDTH - 1 downto 0);
16    wr_data : in std_ulogic_vector(DATA_WIDTH - 1 downto 0)
17  );
18 end entity;
```

HWMoD
WS25

RAM

Introduction
FPGA Memory
Simple DP RAM
True DP RAM
Dual-Clocked RAM
Implementation

Now that we know how RAM interfaces look like, and how to operate them, the question remains how they are actually implemented in VHDL. For RAM in FPGA design, there are two main approaches: instantiating RAM from a vendor library or letting the synthesis tool infer RAM based on the VHDL description. Each approach has its advantages and disadvantages.

RAM Implementation

HWMoD
WS25

RAM

- Introduction
- FPGA Memory
- Simple DP RAM
- True DP RAM
- Dual-Clocked RAM
- Implementation**

Vendor-Library Instantiation

Synthesis Inference

RAM in VHDL (for FPGAs)

Implementation

RAM Implementation

	Vendor-Library Instantiation	Synthesis Inference
Portability/Flexibility	Limited to vendor/device, requires vendor-specific knowledge	Generic and portable, simpler to work with and maintain

Designs which use vendor library components are inherently limited to specific devices or families of devices, which in turn makes these designs less portable. It also requires some level of familiarity with vendor-specific libraries and their configuration options. Furthermore, models for the library components are required for simulation, which can make things more complicated when multiple different simulation tools are used. Inferring memory, directly from VHDL code does not come with these issues and code relying on it is, thus, generally more portable and easier to maintain. It also allows to – for example – describe highly specialized memories that store values of some custom type.

RAM Implementation

HWMoD
WS25

RAM
Introduction
FPGA Memory
Simple DP RAM
True DP RAM
Dual-Clocked RAM
Implementation

	Vendor-Library Instantiation	Synthesis Inference
Portability/Flexibility	Limited to vendor/device, requires vendor-specific knowledge	Generic and portable, simpler to work with and maintain

RAM in VHDL (for FPGAs)

Implementation

RAM Implementation

	Vendor-Library Instantiation	Synthesis Inference
Portability/Flexibility	Limited to vendor/device, requires vendor-specific knowledge	Generic and portable, simpler to work with and maintain
Performance	Optimized for target hardware	May be suboptimal

On the other hand, instantiating library components can offer better performance in certain situations, as the designer has more direct control over the generated hardware. It also makes it possible to force the synthesis tool to use certain specific hardware resources in an FPGA. For the inference of memories during synthesis one has to be careful. When the description does not match the structure required for the available memory blocks, the performance can be severely impeded. However, there is no guarantee that this always leads to a performance hit or otherwise problematic hardware. Therefore, it is always a good idea to check if the hardware generated by the synthesis tool matches the memory you believe you described.

RAM Implementation

HWMoD
WS25

RAM
Introduction
FPGA Memory
Simple DP RAM
True DP RAM
Dual-Clocked RAM
Implementation

	Vendor-Library Instantiation	Synthesis Inference
Portability/Flexibility	Limited to vendor/device, requires vendor-specific knowledge	Generic and portable, simpler to work with and maintain
Performance	Optimized for target hardware	May be suboptimal

RAM in VHDL (for FPGAs)

Implementation

RAM Implementation

	Vendor-Library Instantiation	Synthesis Inference
Portability/Flexibility	Limited to vendor/device, requires vendor-specific knowledge	Generic and portable, simpler to work with and maintain
Performance	Optimized for target hardware	May be suboptimal
Special Features	Fully supported (e.g., ECC)	May be unavailable

Furthermore, in some cases there might be no other way than instantiating library components, as it might be the only way to access certain special hardware features, like error-detection.

RAM Implementation

HWMoD
WS25

RAM
Introduction
FPGA Memory
Simple DP RAM
True DP RAM
Dual-Clocked RAM
Implementation

	Vendor-Library Instantiation	Synthesis Inference
Portability/Flexibility	Limited to vendor/device, requires vendor-specific knowledge	Generic and portable, simpler to work with and maintain
Performance	Optimized for target hardware	May be suboptimal
Special Features	Fully supported (e.g., ECC)	May be unavailable

RAM in VHDL (for FPGAs)

Implementation

RAM Implementation

	Vendor-Library Instantiation	Synthesis Inference
Portability/Flexibility	Limited to vendor/device, requires vendor-specific knowledge	Generic and portable, simpler to work with and maintain
Performance	Optimized for target hardware	May be suboptimal
Special Features	Fully supported (e.g., ECC)	May be unavailable
Predictability	Deterministic	May cause mismatch in synthesis/simulation tool

Finally, predictability is a significant factor as well. Synthesis inference can sometimes lead to mismatches between synthesis and simulation tools, which may introduce challenges during verification. Specifically in edge cases, where the same memory location is read and written at the same time.

RAM Implementation

HWMoD
WS25

RAM
Introduction
FPGA Memory
Simple DP RAM
True DP RAM
Dual-Clocked RAM
Implementation

	Vendor-Library Instantiation	Synthesis Inference
Portability/Flexibility	Limited to vendor/device, requires vendor-specific knowledge	Generic and portable, simpler to work with and maintain
Performance	Optimized for target hardware	May be suboptimal
Special Features	Fully supported (e.g., ECC)	May be unavailable
Predictability	Deterministic	May cause mismatch in synthesis/simulation tool

RAM in VHDL (for FPGAs)

Implementation

Inferred RAM

```
1 architecture beh of simple_dp_ram is
2   subtype ram_entry_t is std_ulogic_vector(DATA_WIDTH - 1 downto 0);
3   type ram_t is array(0 to (2 ** ADDR_WIDTH) - 1) of ram_entry_t;
4   signal ram : ram_t := (others => (others => '0'));
5 begin
6   process (clk)
7   begin
8     if rising_edge(clk) then
9       if wr_en = '1' then
10        ram(to_integer(unsigned(wr_addr))) <= wr_data;
11      end if;
12      if rd_en = '1' then
13        rd_data <= ram(to_integer(unsigned(rd_addr)));
14      end if;
15    end if;
16  end process;
17 end architecture;
```

Finally, let's look at some VHDL code that can be used to infer RAM. Here, we see a possible architecture implementation for the simple dual-port RAM.

Inferred RAM

```
1 architecture beh of simple_dp_ram is
2   subtype ram_entry_t is std_ulogic_vector(DATA_WIDTH - 1 downto 0);
3   type ram_t is array(0 to (2 ** ADDR_WIDTH) - 1) of ram_entry_t;
4   signal ram : ram_t := (others => (others => '0'));
5 begin
6   process (clk)
7   begin
8     if rising_edge(clk) then
9       if wr_en = '1' then
10        ram(to_integer(unsigned(wr_addr))) <= wr_data;
11      end if;
12      if rd_en = '1' then
13        rd_data <= ram(to_integer(unsigned(rd_addr)));
14      end if;
15    end if;
16  end process;
17 end architecture;
```

HWMoD
WS25

RAM

Introduction
FPGA Memory
Simple DP RAM
True DP RAM
Dual-Clocked RAM
Implementation

RAM in VHDL (for FPGAs)

Implementation

Inferred RAM

```
1 architecture beh of simple_dp_ram is
2   subtype ram_entry_t is std_ulogic_vector(DATA_WIDTH - 1 downto 0);
3   type ram_t is array(0 to (2 ** ADDR_WIDTH) - 1) of ram_entry_t;
4   signal ram : ram_t := (others => (others => '0'));
5 begin
6   if rd_en = '1' then
7     ram(to_integer(unsigned(rd_addr))) <= wr_data;
8   end if;
9   if rd_en = '1' then
10    rd_data <= ram(to_integer(unsigned(rd_addr)));
11  end if;
12 end process;
13 end architecture;
```

Use parentheses and signal reference for the signal that actually represents the memory array.

First some types and the signal that actually represents the memory array are declared.

Inferred RAM

```
1 architecture beh of simple_dp_ram is
2   subtype ram_entry_t is std_ulogic_vector(DATA_WIDTH - 1 downto 0);
3   type ram_t is array(0 to (2 ** ADDR_WIDTH) - 1) of ram_entry_t;
4   signal ram : ram_t := (others => (others => '0'));
5 begin
6   process (clk)
7   begin
8     if rising_edge(clk) then
9       if wr_en = '1' then
10        ram(to_integer(unsigned(wr_addr))) <= wr_data;
11      end if;
12      if rd_en = '1' then
13        rd_data <= ram(to_integer(unsigned(rd_addr)));
14      end if;
15    end if;
16  end process;
17 end architecture;
```

Type definitions and signal declaration for the signal that actually represents the memory array.

HWMoD
WS25

RAM
Introduction
FPGA Memory
Simple DP RAM
True DP RAM
Dual-Clocked RAM
Implementation

RAM in VHDL (for FPGAs)

Implementation

Inferred RAM

```
1 architecture beh of simple_dp_ram is
2   subtype ram_entry_t is std_ulogic_vector(DATA_WIDTH - 1 downto 0);
3   type ram_t is array(0 to (2 ** ADDR_WIDTH) - 1) of ram_entry_t;
4   signal ram : ram_t := (others => (others => '0'));
5 begin
6   process (clk)
7   begin
8     if rising_edge(clk) then
9       if wr_en = '1' then
10        ram(to_integer(unsigned(wr_addr))) <= wr_data;
11      end if;
12      if rd_en = '1' then
13        rd_data <= ram(to_integer(unsigned(rd_addr)));
14      end if;
15    end if;
16  end process;
17 end architecture;
```

Synchronous process similar to what is used in the description of flip-flops.

Since we are describing synchronous RAM, we need a process whose body is only executed on rising clock edges.

Inferred RAM

```
1 architecture beh of simple_dp_ram is
2   subtype ram_entry_t is std_ulogic_vector(DATA_WIDTH - 1 downto 0);
3   type ram_t is array(0 to (2 ** ADDR_WIDTH) - 1) of ram_entry_t;
4   signal ram : ram_t := (others => (others => '0'));
5 begin
6   process (clk)
7   begin
8     if rising_edge(clk) then
9       if wr_en = '1' then
10        ram(to_integer(unsigned(wr_addr))) <= wr_data;
11      end if;
12      if rd_en = '1' then
13        rd_data <= ram(to_integer(unsigned(rd_addr)));
14      end if;
15    end if;
16  end process;
17 end architecture;
```

Synchronous process similar to what is used in the description of flip-flops.

HWMoD
WS25

RAM
Introduction
FPGA Memory
Simple DP RAM
True DP RAM
Dual-Clocked RAM
Implementation

RAM in VHDL (for FPGAs)

Implementation

Inferred RAM

```
1 architecture beh of simple_dp_ram is
2   subtype ram_entry_t is std_ulogic_vector(DATA_WIDTH - 1 downto 0);
3   type ram_t is array(0 to (2 ** ADDR_WIDTH) - 1) of ram_entry_t;
4   signal ram : ram_t := (others => (others => '0'));
5 begin
6   if rd_en = '1' then
7     ram(to_integer(unsigned(rd_addr))) <= wr_data;
8   end if;
9   if rd_en = '1' then
10    rd_data <= ram(to_integer(unsigned(rd_addr)));
11  end if;
12 end process;
13 end architecture;
```

In the process body the write-port is implemented by first checking the write-enable signal. If this signal is asserted, the address is used to index the memory array.

Inferred RAM

HWMoD
WS25

RAM
Introduction
FPGA Memory
Simple DP RAM
True DP RAM
Dual-Clocked RAM
Implementation

```
1 architecture beh of simple_dp_ram is
2   subtype ram_entry_t is std_ulogic_vector(DATA_WIDTH - 1 downto 0);
3   type ram_t is array(0 to (2 ** ADDR_WIDTH) - 1) of ram_entry_t;
4   signal ram : ram_t := (others => (others => '0'));
5 begin
6   process (clk)
7   begin
8     if rising_edge(clk) then
9       if wr_en = '1' then
10        ram(to_integer(unsigned(wr_addr))) <= wr_data;
11      end if;
12      if rd_en = '1' then
13        rd_data <= ram(to_integer(unsigned(rd_addr)));
14      end if;
15    end if;
16  end process;
17 end architecture;
```

Implementation of the write port.

Thank you for listening! We recommend you to immediately take the self-check test in TUWEL, to see if you understood the material presented in this lecture.

HWMoD
WS25

RAM

Introduction
FPGA Memory
Simple DP RAM
True DP RAM
Dual-Clocked RAM
Implementation

Lecture Complete!